

# BASIC ELECTRICAL ENGINEERING

Course Code: EE100



**Dr. Pragnyashree Ray**

Assistant Professor

Dept. of Electrical Engineering,

C. V. Raman Global University, Bhubaneswar, Odisha

# Module 1: DC Circuits

## Theorems

- ✓ **Superposition Theorem**
- ✓ **Thevenin's Theorem**
- ✓ **Norton's Theorem**
- ✓ **Maximum Power transfer Theorem**





# Superposition Theorem


In a **linear, bilateral d.c.** network containing **more than one energy** source, the **resultant** potential difference across or current through any element is equal to the **algebraic sum** of potential differences or currents for that element produced by each source acting alone with all **voltage sources** replaced by **short circuits** and **current sources** replaced by **open circuits**.



# Superposition Theorem

## Procedure for Superposition Theorem

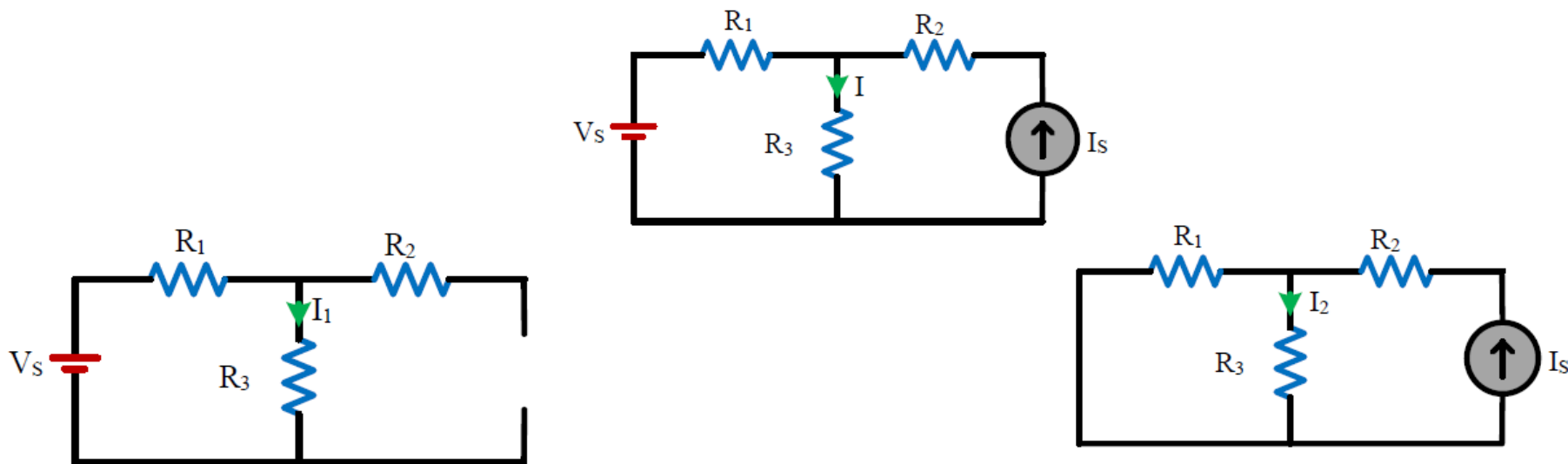1. Select one source in the circuit and replace all other voltage sources by short circuits and current sources by open circuits.
2. Determine the voltage across or current through the desired element/branch due to single source selected in step 1.
3. Repeat the above two steps for each of the remaining sources.
4. Algebraically add all the voltages across or currents through the element/branch under consideration. The sum is the actual voltage across or current through that element/branch when all the sources are acting simultaneously.





$$I = I_1 + I_2$$



# Thevenin's Theorem

**Any linear, bilateral network having terminals A and B can be replaced by a single source of e.m.f.  $V_{Th}$  in series with a single resistance  $R_{Th}$ .**

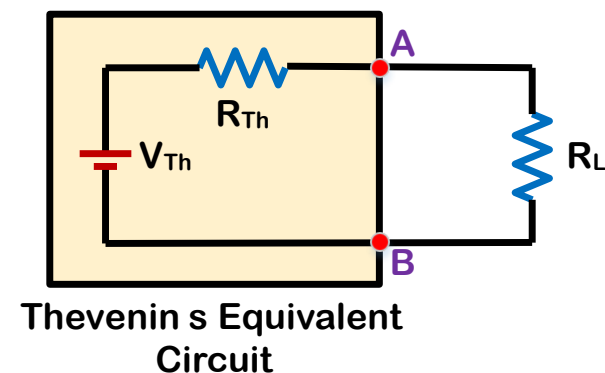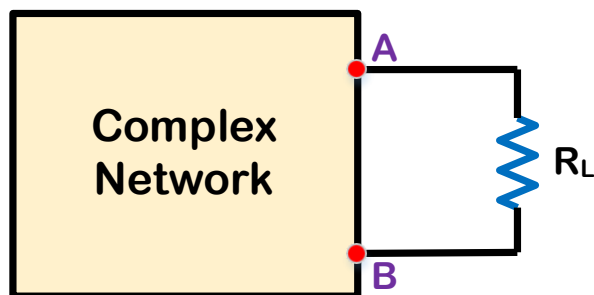- (i) The e.m.f.  $V_{Th}$  is the voltage obtained across terminals A and B with load, if any removed i.e. it is open-circuited voltage between terminals A and B.
- (ii) The resistance  $R_{Th}$  is the resistance of the network measured between terminals A and B with load removed and sources of e.m.f. replaced by their internal resistances. Voltage sources are replaced with short circuits and current sources are replaced with open circuits.







# Thevenin's Theorem


## Procedure for Finding Thevenin Equivalent Circuit

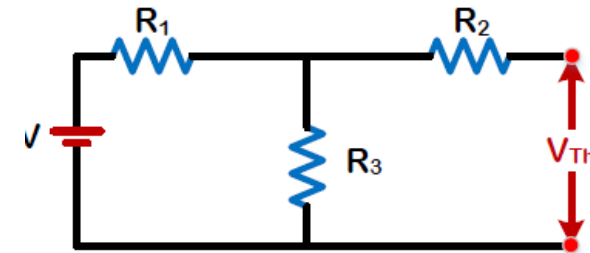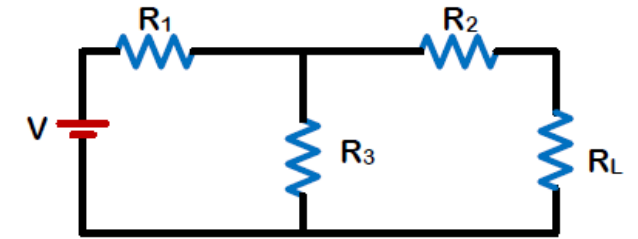1. Open the two terminals (i.e., remove any load) between which you want to find Thevenin equivalent circuit.
2. Find the open-circuit voltage between the two open terminals. It is called Thevenin voltage  $V_{Th}$ .
3. Determine the resistance between the two open terminals with all voltage sources shorted and all current sources opened. It is called Thevenin resistance  $R_{Th}$ .
4. Connect  $V_{Th}$  and  $R_{Th}$  in series to produce Thevenin equivalent circuit between the two terminals under consideration.
5. Place the load resistor removed in step (1) across the terminals of the Thevenin equivalent circuit. The load current can now be calculated using only Ohm's law and it has the same value as the load current in the original circuit.




$V_{Th} = \text{Voltage across } R_3$

$$V_{Th} = \frac{V}{R_1 + R_3} R_3$$

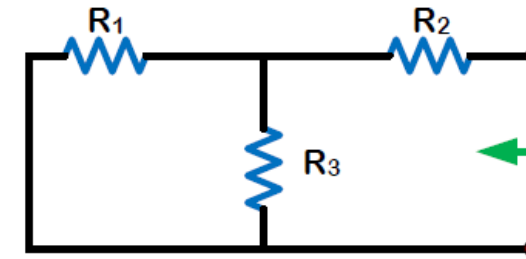

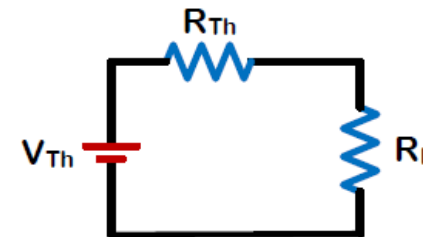$R_{Th} = R_2 + \frac{R_1 R_3}{R_1 + R_3}$




$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$


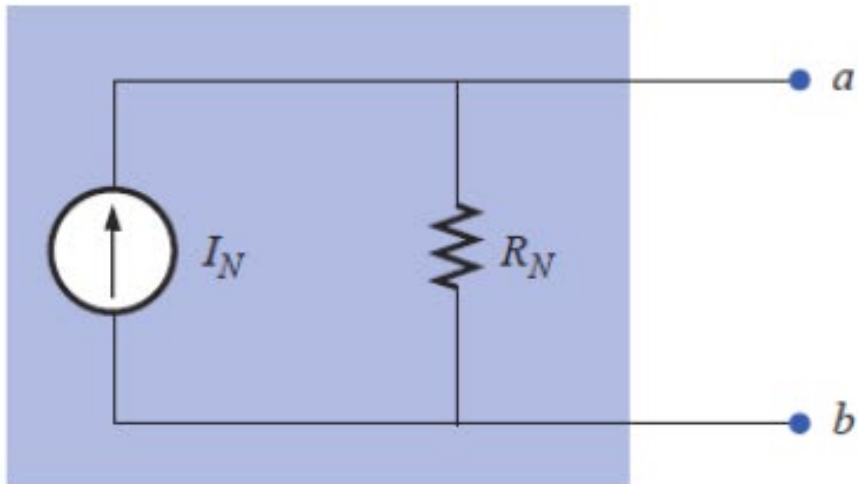
# Nortons Theorem

*Any two-terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current source and a parallel resistor, as shown in Fig.*







# Nortons Theorem

1. *Remove the portion of the network across which the Norton equivalent circuit is to be found.*
2. *Mark the terminals of the remaining two-terminal network.*

$R_N$ :

3. *Calculate  $R_N$  by first setting all sources to zero (voltage sources are replaced by short circuits, and current sources by open circuits) and then finding the resultant resistance between the two marked terminals. (If the internal resistance of the voltage and/or current sources is included in the original network, it must remain when the sources are set to zero.) Since  $R_N = R_{Th}$ , the procedure and value obtained using the approach described for Thévenin's theorem will determine the proper value of  $R_N$ .*

$I_N$ :

4. *Calculate  $I_N$  by first returning all sources to their original position and finding the short-circuit current between the marked terminals.*


**Conclusion:**

5. *Draw the Norton equivalent circuit with the portion of the circuit previously removed replaced between the terminals of the equivalent circuit.*






# Nortons Theorem

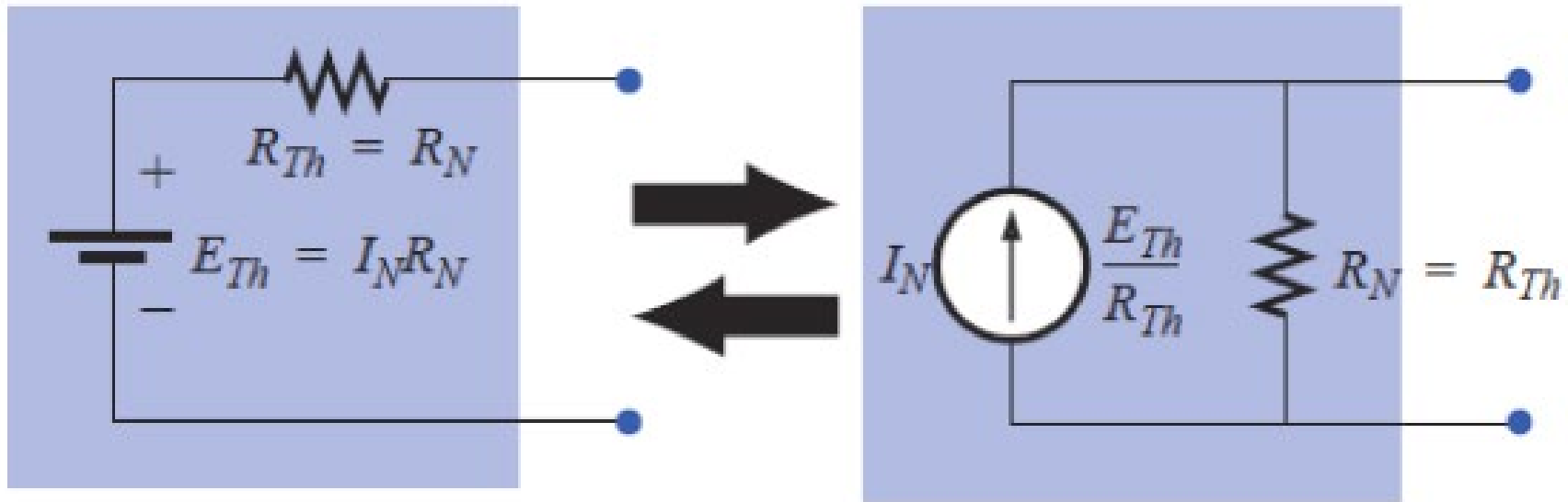

*Converting between Thévenin and Norton equivalent circuits.*
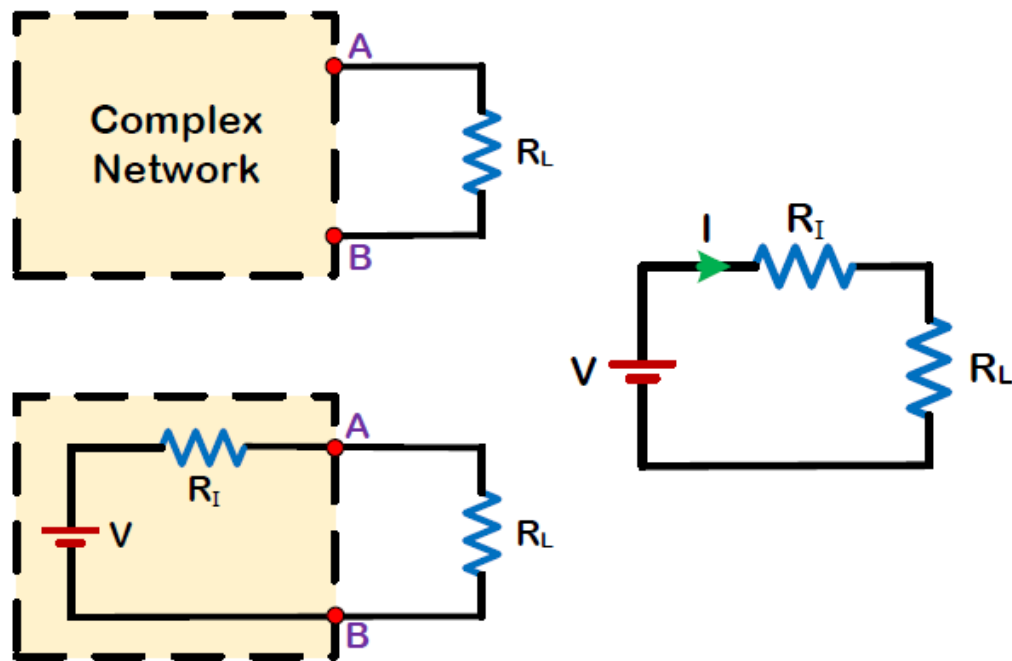
# Maximum Power Transfer Theorem

In d.c. circuits, maximum power is transferred from a source to load when the load resistance is made equal to the internal resistance of the source as viewed from the load terminals with load removed and all e.m.f. sources replaced by their internal resistances.




$$V = 12V$$

$$R_I = 3\Omega$$

$R_L$	$I = \frac{V}{R_I + R_L}$	Power Delivered to Load $P_L = I^2 * R_L$
1Ω	I=3 A	$P_L = 9\text{ W}$
2Ω	I=2.4 A	$P_L = 11.52\text{ W}$
3Ω	I=2 A	$P_L = 12\text{ W}$
4Ω	I=1.71 A	$P_L = 11.69\text{ W}$
5Ω	I=1.5 A	$P_L = 11.25\text{ W}$
6Ω	I=1.33 A	$P_L = 10.61\text{ W}$

# Maximum Power Transfer Theorem
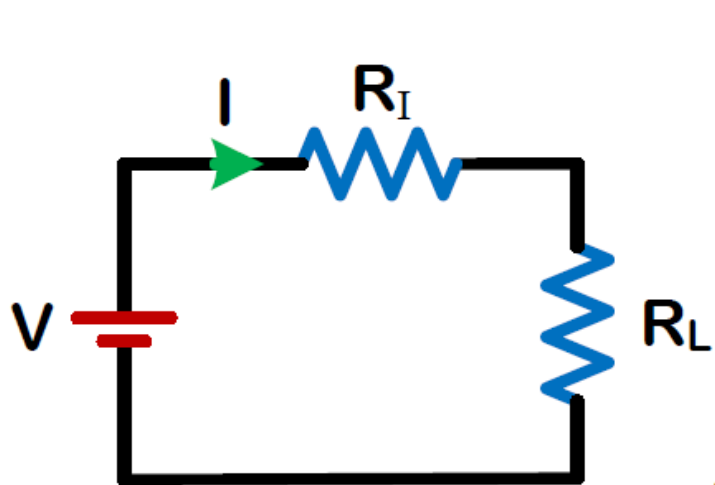
## Proof of Maximum Power Transfer Theorem



$$I = \frac{V}{R_L + R_I}$$

$$P_L = I^2 R_L = \left( \frac{V}{R_L + R_I} \right)^2 R_L$$

$$\frac{dP_L}{dR_L} = V^2 \left[ \frac{(R_L + R_I)^2 - 2R_L(R_L + R_I)}{(R_L + R_I)^4} \right] = 0$$

$$(R_L + R_I)^2 - 2R_L(R_L + R_I) = 0$$

$$(R_L + R_I)(R_L + R_I - 2R_L) = 0$$

$$(R_L + R_I)(R_I - R_L) = 0$$

$$(R_L + R_I) \neq 0$$

$$R_I - R_L = 0$$

$$R_L = R_I$$

**Load resistance = Internal resistance**

# Maximum Power Transfer Theorem

## Important Points

- ✓ The circuit efficiency at maximum power transfer is only 50% as one-half of the total power generated is dissipated in the internal resistance  $R_I$  of the source.

$$\eta = \frac{\text{Output Power}}{\text{Input Power}} = \frac{I^2 R_L}{I^2 (R_L + R_I)} = \frac{R_L}{2R_L} = \frac{1}{2} = 50\%$$

- ✓ Under the conditions of maximum power transfer, the load voltage is one-half of the open circuited voltage at the load terminals.

$$V_L = IR_L = \frac{V}{R_L + R_I} R_L = \frac{V}{2}$$

- ✓ Value of maximum power transferred


$$P_{L,max} = \left( \frac{V}{R_L + R_I} \right)^2 R_L = \frac{V^2}{4R_L}$$



# Superposition Theorem

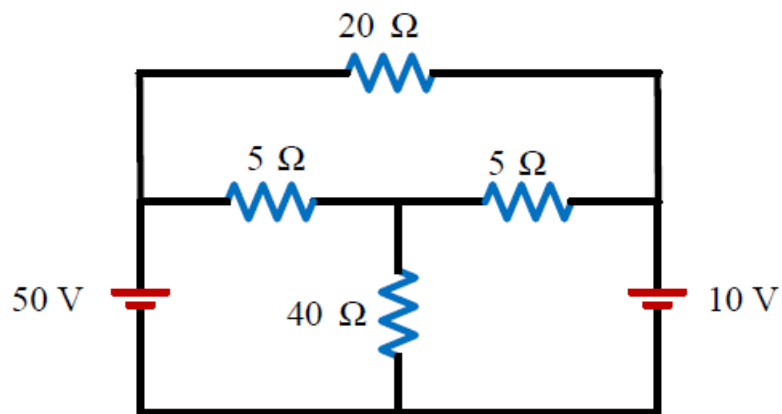
## Example

Using superposition theorem, find the current through the  $40\ \Omega$  resistor in the circuit shown




Solution:

Step 1:

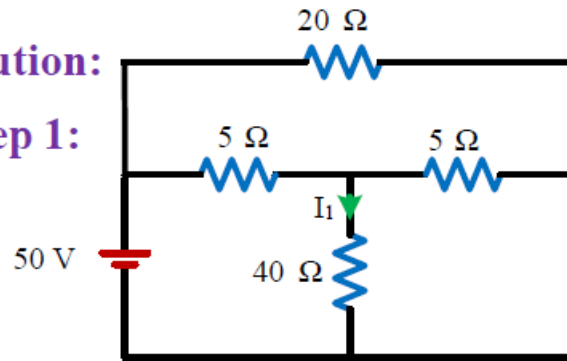


$$I' = \frac{50}{5 + 4.44} = 5.296A$$

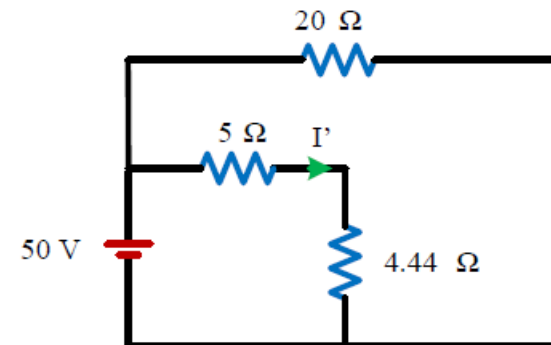


$$I_1 = I' \frac{5}{5 + 40} = 0.589A$$

Step 2:

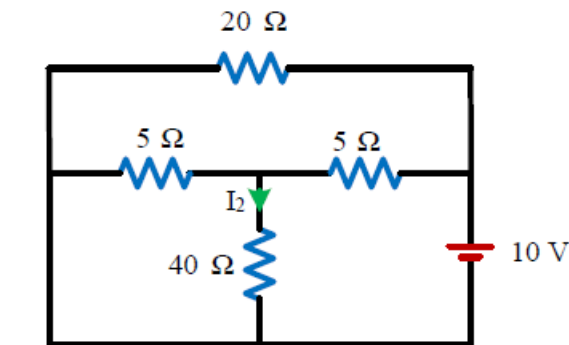

$$I'' = \frac{10}{5 + 4.44} = 1.059A$$

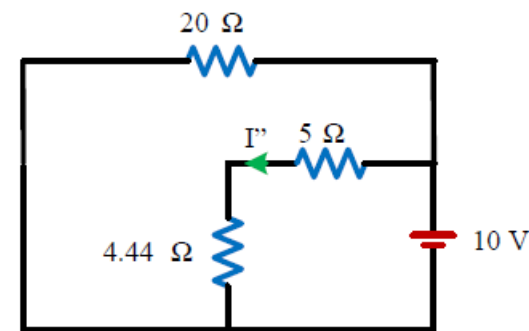


$$I_2 = 1.059 \frac{5}{5 + 40} = 0.118A$$

$$I = I_1 + I_2 = 0.589 + 0.118 = 0.707A$$




# Superposition Theorem

## Example

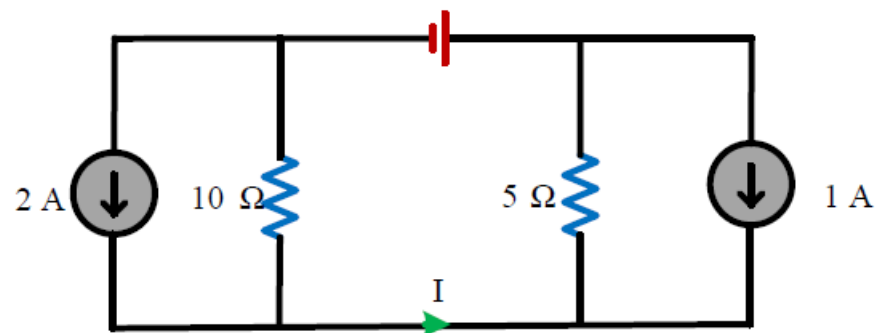


Solution:

Step 1:

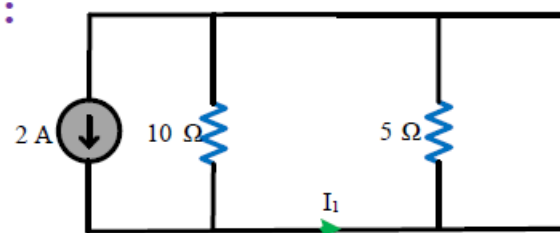


$$I_1 = 2 \frac{10}{5 + 10} = 1.33A$$

Step 2:

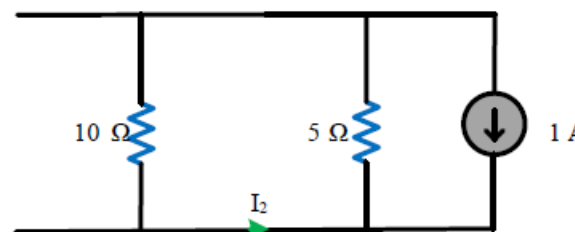

$$I_2 = -1 \frac{5}{5 + 10} = -0.33A$$

Step 3:

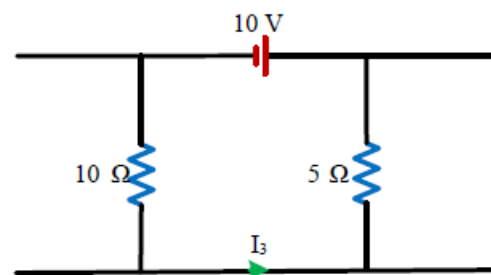

$$I_3 = - \frac{10}{5 + 10} = -0.667A$$

$$I = I_1 + I_2 + I_3 = 0.33A$$






# Superposition Theorem
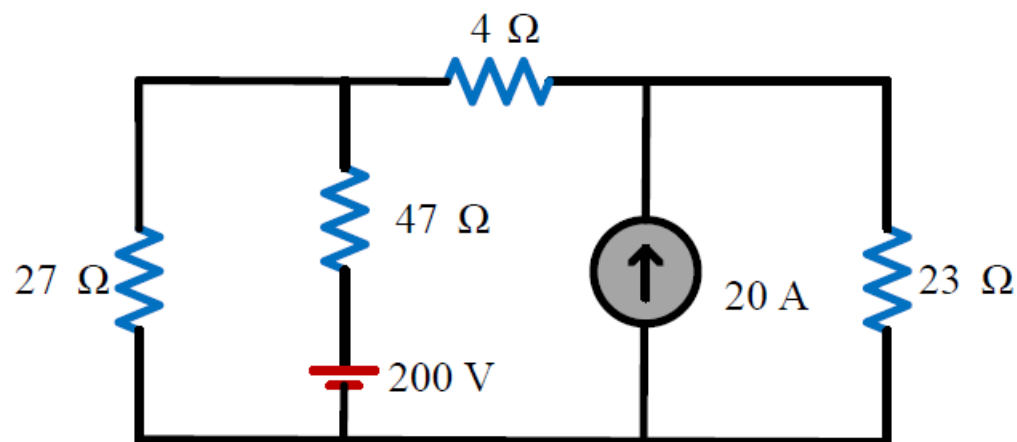
## Tutorial

Using superposition theorem, find the current in  $23\ \Omega$  resistor in the circuit shown



**Solution:**

**200 V source acting alone**

$$I_1 = 1.65A$$

**20 A current source acting alone.**

$$I_2 = 9.58A$$

$$I = I_1 + I_2 = 11.23A$$