

# **BEEE100**

## **Basic Electrical Engineering**

### **Module – 02:** AC Circuits



Three phase balanced



# Three Phase Systems

## Single Phase System

$$e_{a_1a_2} = E_m \sin \omega t$$

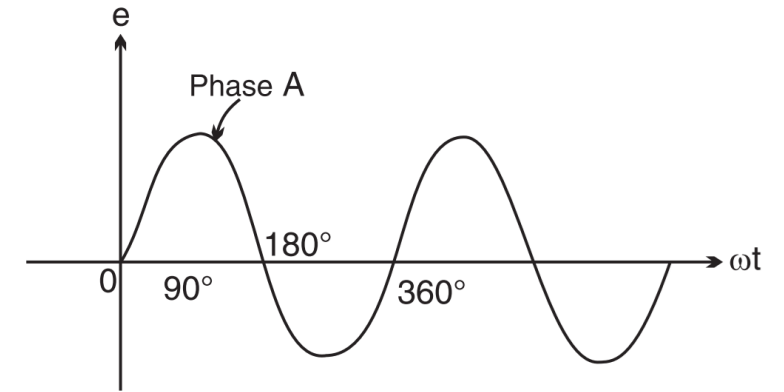
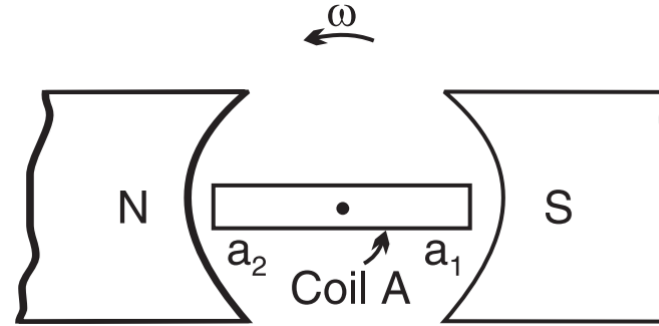


**Circuits or systems in which the ac sources operate at the same frequency but different phases are known as *polyphase***
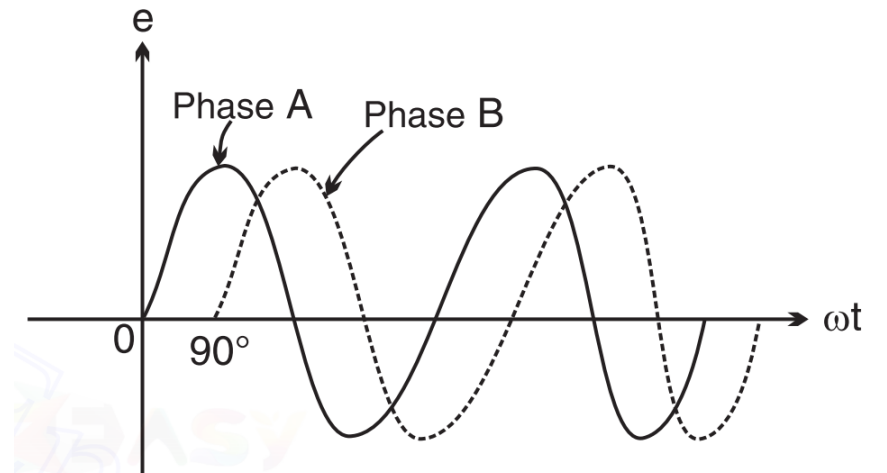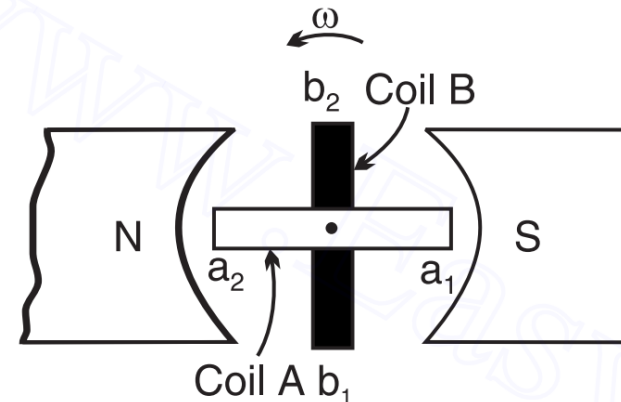
## Two Phase System

$$e_{a_1a_2} = E_m \sin \omega t$$



$$e_{b_1b_2} = E_m \sin(\omega t - 90^\circ)$$





# Three phase systems

## Three Phase System

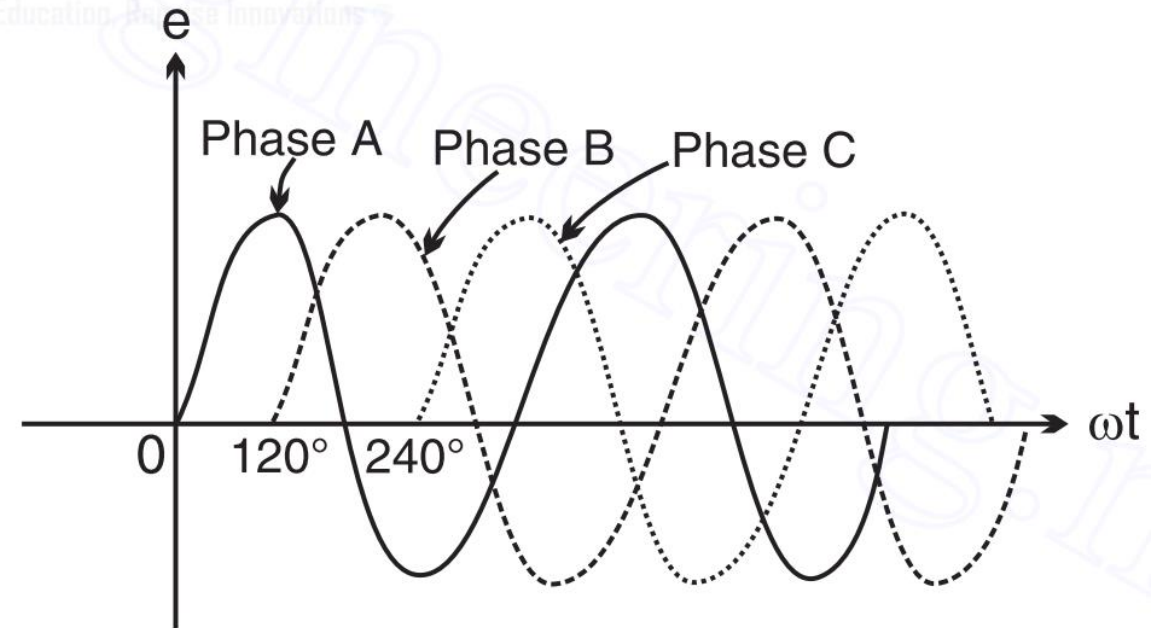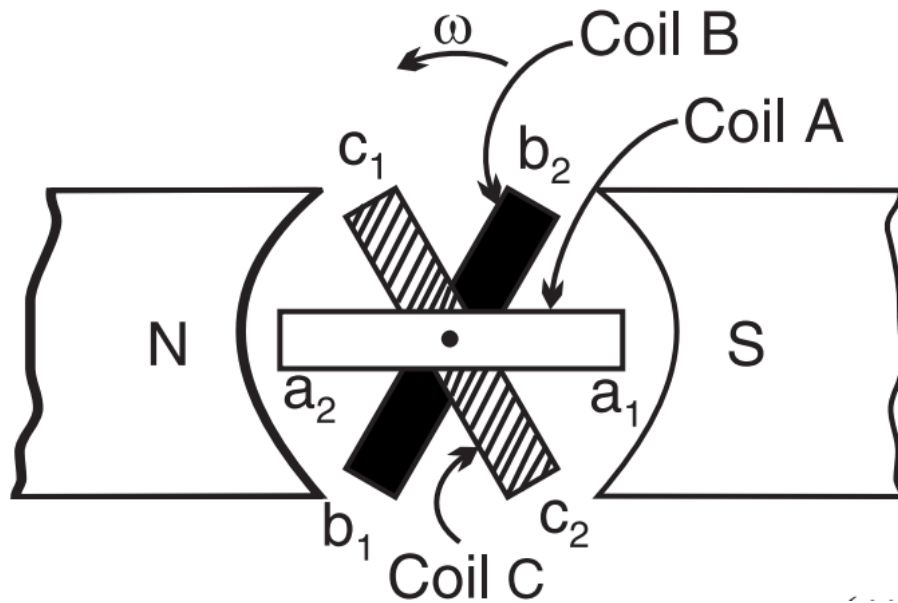

$$e_{a_1a_2} = E_m \sin \omega t$$

$$e_{b_1b_2} = E_m \sin(\omega t - 120^\circ)$$

$$e_{c_1c_2} = E_m \sin(\omega t - 240^\circ)$$





# Three phase systems




## Why Three Phase?

- ❖ **Constant power.** In a single-phase circuit, the instantaneous power varies sinusoidally from zero to a peak value at twice the supply frequency. However, in a balanced 3-phase system, the power supplied at all instants of time is constant.
- ❖ **Greater output.** The output of a 3-phase machine is greater than that of a single-phase machine for a given volume and weight of the machine.
- ❖ **Cheaper.** The three-phase motors are much smaller and less expensive than single-phase motors because less material (copper, iron, insulation) is required.
- ❖ **Power transmission economics.** Transmission of electric power by 3-phase system is cheaper than that of single-phase system, even though three conductors are required instead of two.
- ❖ **Rotating Magnetic Field** A 3-phase system can set-up a rotating uniform magnetic field in stationary windings. This cannot be done with a single-phase current.





# Three phase systems

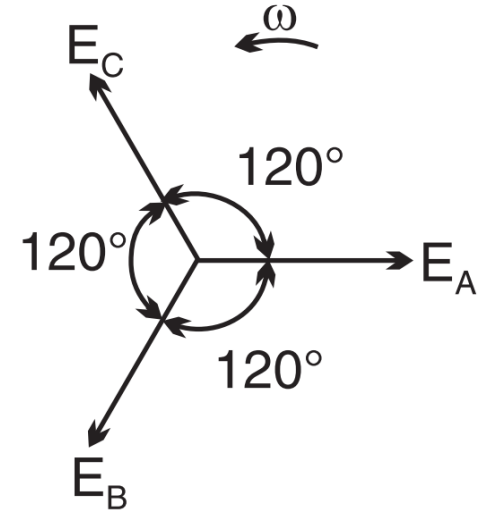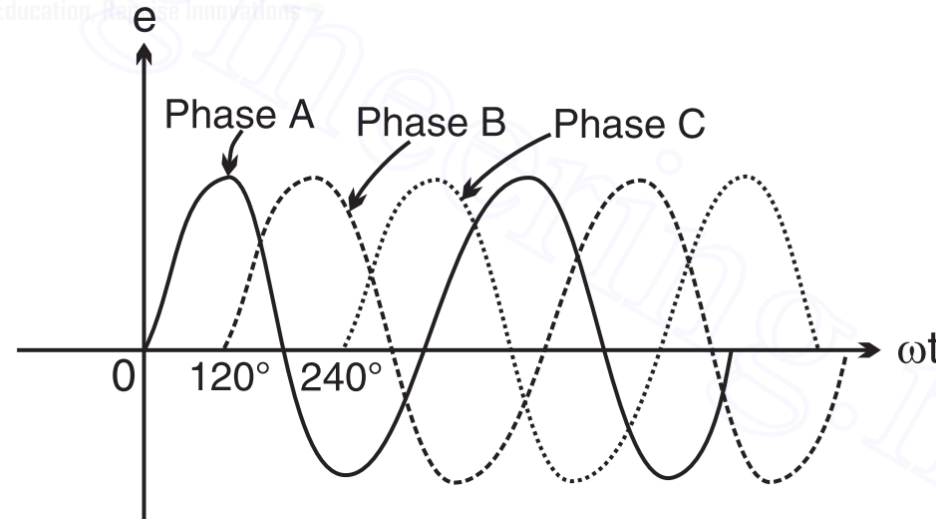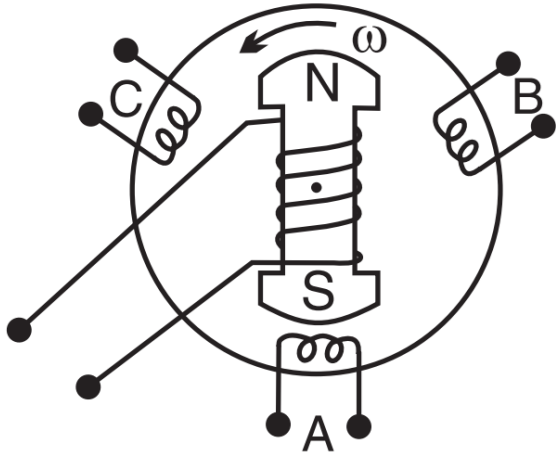

$$e_A = E_m \sin \omega t$$

$$e_B = E_m \sin(\omega t - 120^\circ)$$

$$e_C = E_m \sin(\omega t - 240^\circ) = E_m \sin(\omega t + 120^\circ)$$

$$\text{Resultant} = e_A + e_B + e_C$$

$$= E_m [\sin \omega t + \sin(\omega t - 120^\circ) + \sin(\omega t - 240^\circ)]$$

$$= E_m [\sin \omega t + 2 \sin(\omega t - 180^\circ) \cos 60^\circ]$$

$$= E_m [\sin \omega t - 2 \sin \omega t \cos 60^\circ] = 0$$

It is a usual practice to name the three phases or windings after the three natural colors viz. Red (R), yellow (Y) and blue (B). In that case, the phase sequence is RYB i.e. voltage in phase R attains maximum positive value first, next phase Y and then phase B. It may be noted that there are only two possible phase sequences viz RYB and RBY






# Three phase systems

## Three Phase Configurations


- (i) Star or Wye (Y) connection
- (ii) Delta (D) connection

### Y-connection

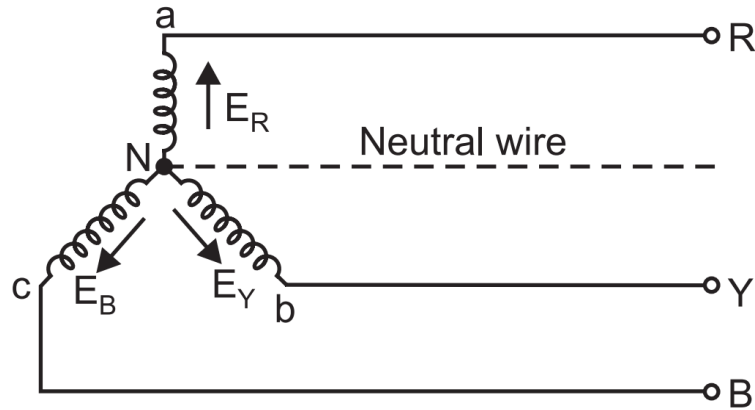

If a neutral conductor exists, the system is called *3-phase, 4 wire system*. If there is no neutral conductor, it is called *3-phase, 3-wire system*.

### D-connection

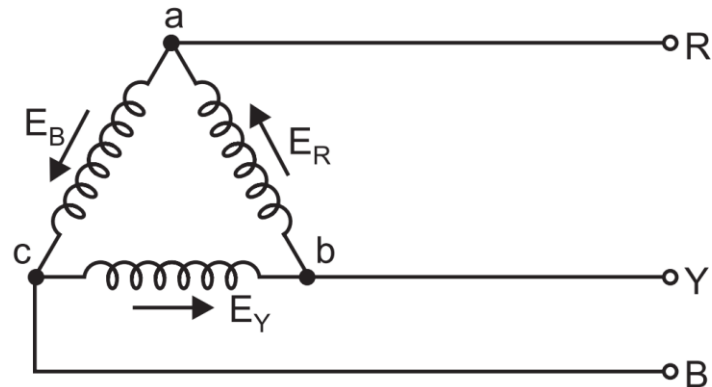


*In a D-connection, no neutral point exists and only 3-phase, 3-wire system can be formed.*





# Three phase systems

## Star or Wye Connected System

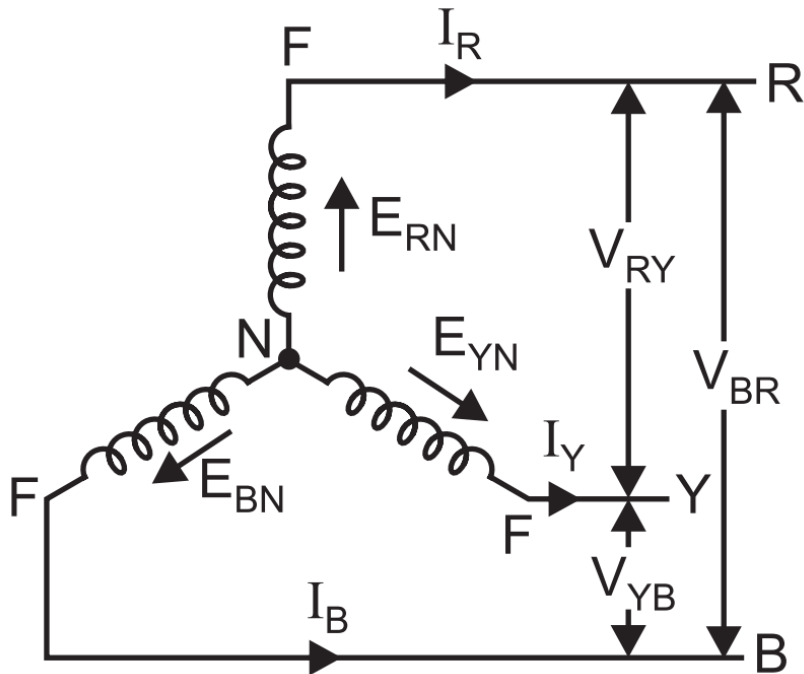

The voltages  $E_{RN}$ ,  $E_{YN}$ , and  $E_{BN}$  are respectively between lines  $R$ ,  $Y$ , and  $B$ , and the neutral line  $N$ . These voltages are called *phase voltages*. If the voltage sources have the same amplitude and frequency  $\omega$  and are out of phase with each other by  $120^\circ$ , the voltages are said to be *balanced*.

### Phase Voltage

$$E_{RN} = V_{Ph} \angle 0^\circ \quad E_{YN} = V_{Ph} \angle -120^\circ$$

$$E_{BN} = V_{Ph} \angle -240^\circ$$

When voltages are balanced

$$E_{RN} + E_{YN} + E_{BN} = 0$$

$$|E_{RN}| = |E_{YN}| = |E_{BN}| = V_{Ph}$$

### Line Voltage

$$V_{RY} = V_L \angle 0^\circ \quad V_{YB} = V_L \angle -120^\circ$$

$$V_{BR} = V_L \angle -240^\circ$$

$$\text{Line voltage} = \sqrt{3} \times \text{Phase voltage}$$

$$V_L = \sqrt{3} V_{Ph}$$

$$\text{Line current} = \text{Phase current}$$



$$I_L = I_{Ph}$$





# Three phase systems

## Star or Wye Connected System

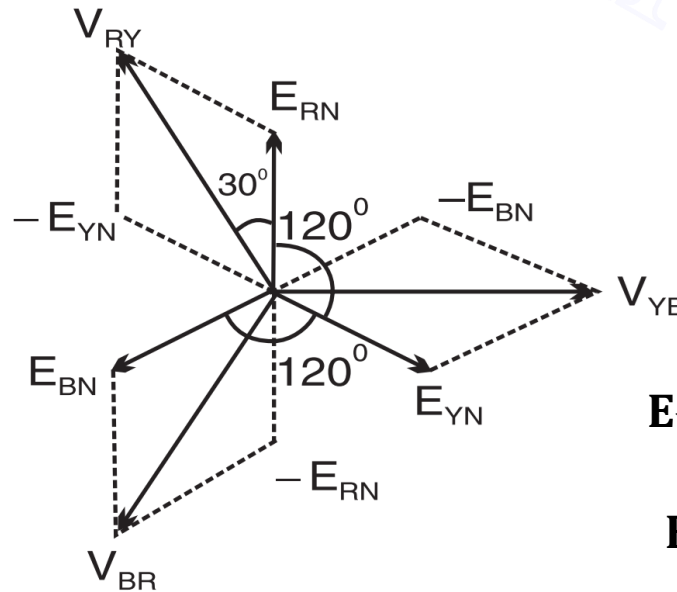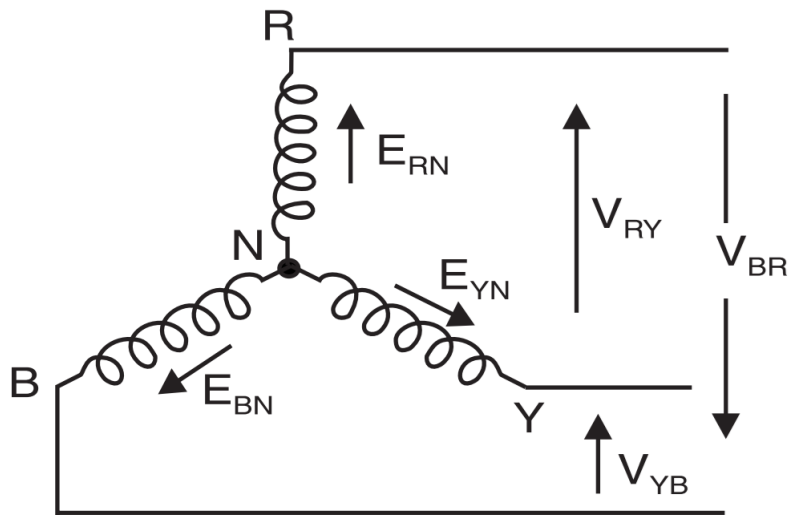

$$V_{RY} = E_{RN} + E_{NY} = E_{RN} - E_{YN}$$

$$V_{RY} = 2V_{Ph} \cos(60^\circ/2) = 2V_{Ph} \cos 30^\circ = \sqrt{3}V_{Ph}$$

$$V_{YB} = E_{YN} - E_{BN} = \sqrt{3}V_{Ph}$$

$$V_{BR} = E_{BN} - E_{RN} = \sqrt{3}V_{Ph}$$

$$\mathbf{E}_{RN} = V_{Ph} \angle 0^\circ = V_{Ph}(1 + j0)$$

$$\mathbf{E}_{YN} = V_{Ph} \angle -120^\circ = V_{Ph}(-0.5 - j0.866)$$

$$\mathbf{E}_{BN} = V_{Ph} \angle -240^\circ = V_{Ph}(-0.5 + j0.866)$$

$$\mathbf{V}_{RY} = \mathbf{E}_{RN} - \mathbf{E}_{YN} = V_{Ph}(1 + j0) - V_{Ph}(-0.5 - j0.866)$$

$$\mathbf{V}_{RY} = V_{Ph}(1.5 + j0.866) = \sqrt{3}V_{Ph} \angle 30^\circ$$








# Three phase systems

## Delta Connected System

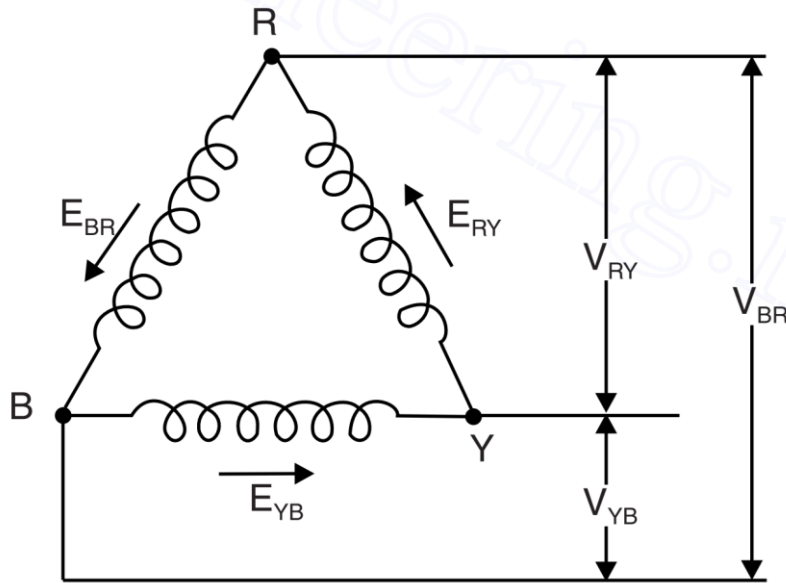

*When voltages are balanced*

$$\mathbf{E}_{RY} = V_{Ph} \angle 0^\circ = V_{Ph}(1 + j0)$$

$$\mathbf{E}_{YB} = V_{Ph} \angle -120^\circ = V_{Ph}(-0.5 - j0.866)$$

$$\mathbf{E}_{BR} = V_{Ph} \angle -240^\circ = V_{Ph}(-0.5 + j0.866)$$

$$\mathbf{E}_{RY} + \mathbf{E}_{YB} + \mathbf{E}_{BR} = V_{Ph}(1 + j0) + V_{Ph}(-0.5 - j0.866) + V_{Ph}(-0.5 + j0.866) = 0$$

Line voltage = Phase voltage

$$V_L = V_{Ph}$$

Line current =  $\sqrt{3} \times$  Phase current



$$I_L = \sqrt{3} I_{Ph}$$





# Three phase systems

## Delta Connected System

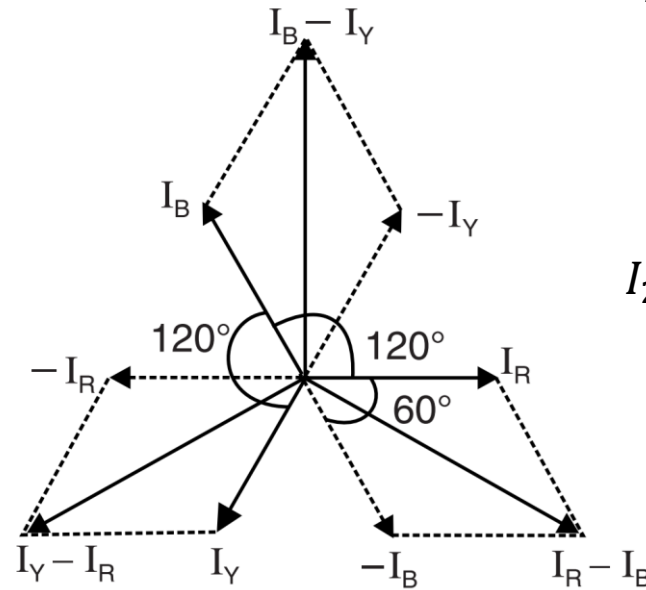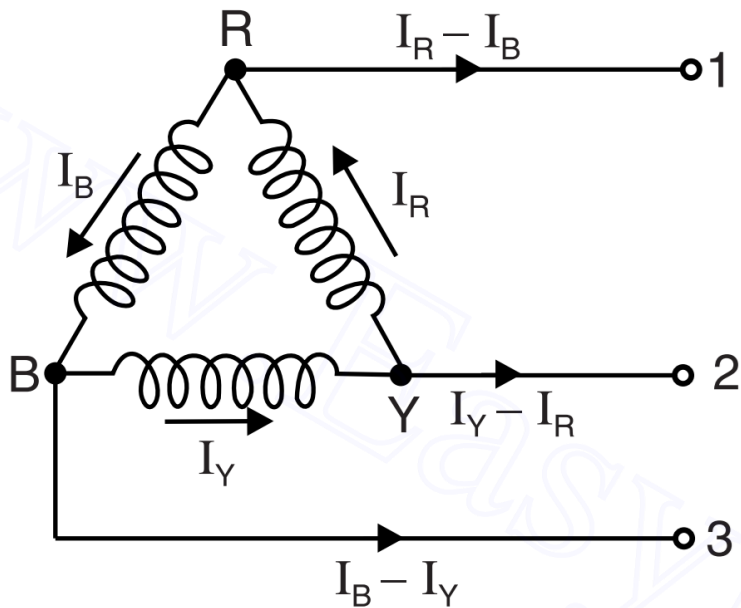

$$I_1 = I_R - I_B \quad I_2 = I_Y - I_R \quad I_3 = I_B - I_Y$$

$$I_1 = 2I_{Ph} \cos(60^\circ/2) = 2I_{Ph} \cos 30^\circ = \sqrt{3}I_{Ph}$$

$$I_2 = I_Y - I_R = \sqrt{3}I_{Ph} \quad I_3 = I_B - I_Y = \sqrt{3}I_{Ph}$$

$$\mathbf{I}_R = I_{Ph} \angle 0^\circ = I_{Ph}(1 + j0)$$

$$\mathbf{I}_Y = I_{Ph} \angle -120^\circ = I_{Ph}(-0.5 - j0.866)$$

$$\mathbf{I}_B = I_{Ph} \angle -240^\circ = I_{Ph}(-0.5 + j0.866)$$

$$\mathbf{I}_1 = \mathbf{I}_R - \mathbf{I}_B = I_{Ph}(1 + j0) - I_{Ph}(-0.5 + j0.866)$$







# Three phase systems

## Three Phase Load

### Star or Y-connected Load

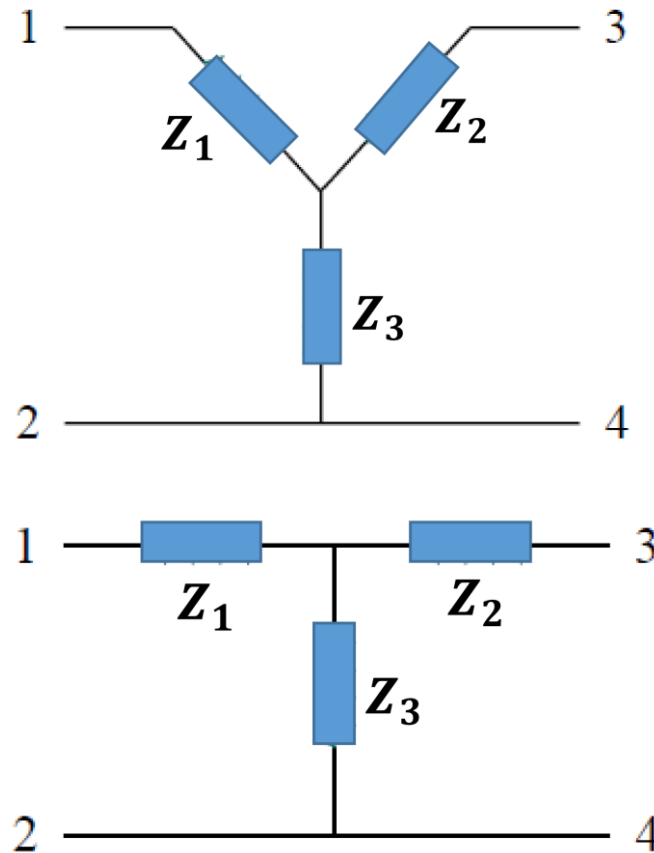


### $\Delta$ -connected Load

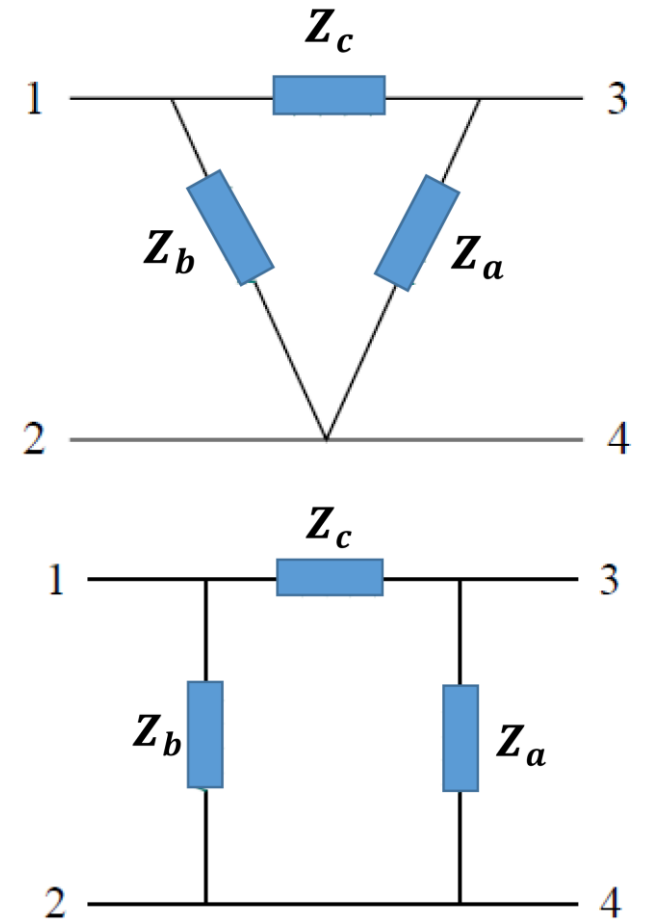



# Three phase systems

## Delta to Wye Conversion

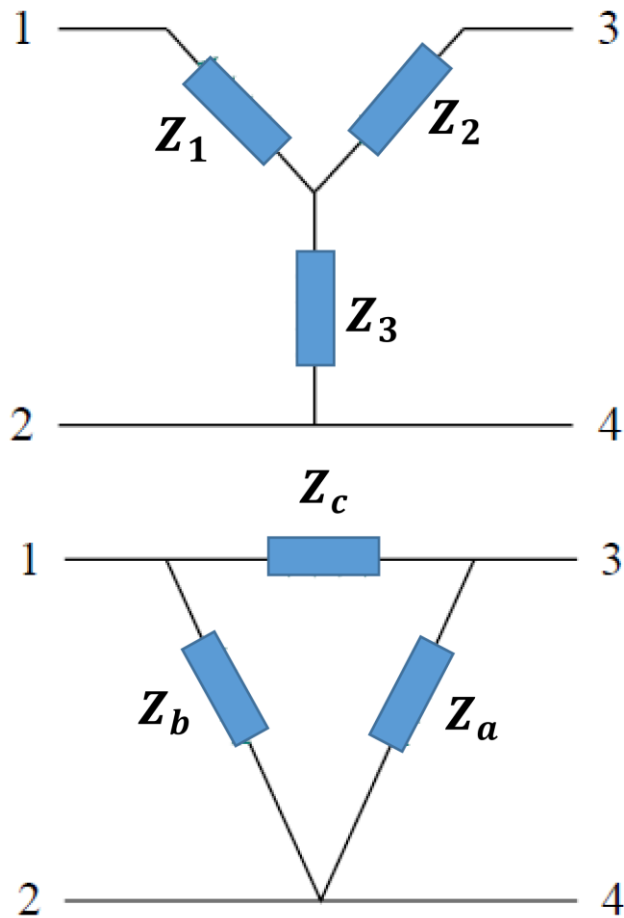

$$Z_{12}(Y) = Z_1 + Z_3$$

$$Z_{12}(\Delta) = Z_b || (Z_a + Z_c)$$

$$Z_{12}(Y) = Z_{12}(\Delta)$$

$$Z_{12} = Z_1 + Z_3 = \frac{Z_b(Z_a + Z_c)}{Z_a + Z_b + Z_c}$$

$$Z_{13} = Z_1 + Z_2 = \frac{Z_c(Z_a + Z_b)}{Z_a + Z_b + Z_c}$$

$$Z_{34} = Z_2 + Z_3 = \frac{Z_a(Z_b + Z_c)}{Z_a + Z_b + Z_c}$$

Subtracting  $Z_{34}$  from  $Z_{12}$

$$Z_1 - Z_2 = \frac{Z_c(Z_b - Z_a)}{Z_a + Z_b + Z_c}$$

Adding  $Z_{13}$  and  $(Z_1 - Z_2)$  gives

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$$\begin{aligned} Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1 &= \frac{Z_a Z_b Z_c (Z_a + Z_b + Z_c)}{(Z_a + Z_b + Z_c)^2} \\ &= \frac{Z_a Z_b Z_c}{(Z_a + Z_b + Z_c)} \end{aligned}$$

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$





# Three phase systems

## Three Phase Load

A **balanced load** is one in which the phase impedances are equal in magnitude and in phase.

For a *balanced wye-connected load*

$$Z_1 = Z_2 = Z_3 = Z_Y$$

where  $Z_Y$  is the load impedance per phase in this case

For a *balanced delta-connected load*

$$Z_a = Z_b = Z_c = Z_\Delta$$

where  $Z_\Delta$  is the load impedance per phase in this case

$$Z_\Delta = 3Z_Y$$


$$Z_Y = \frac{Z_\Delta}{3}$$




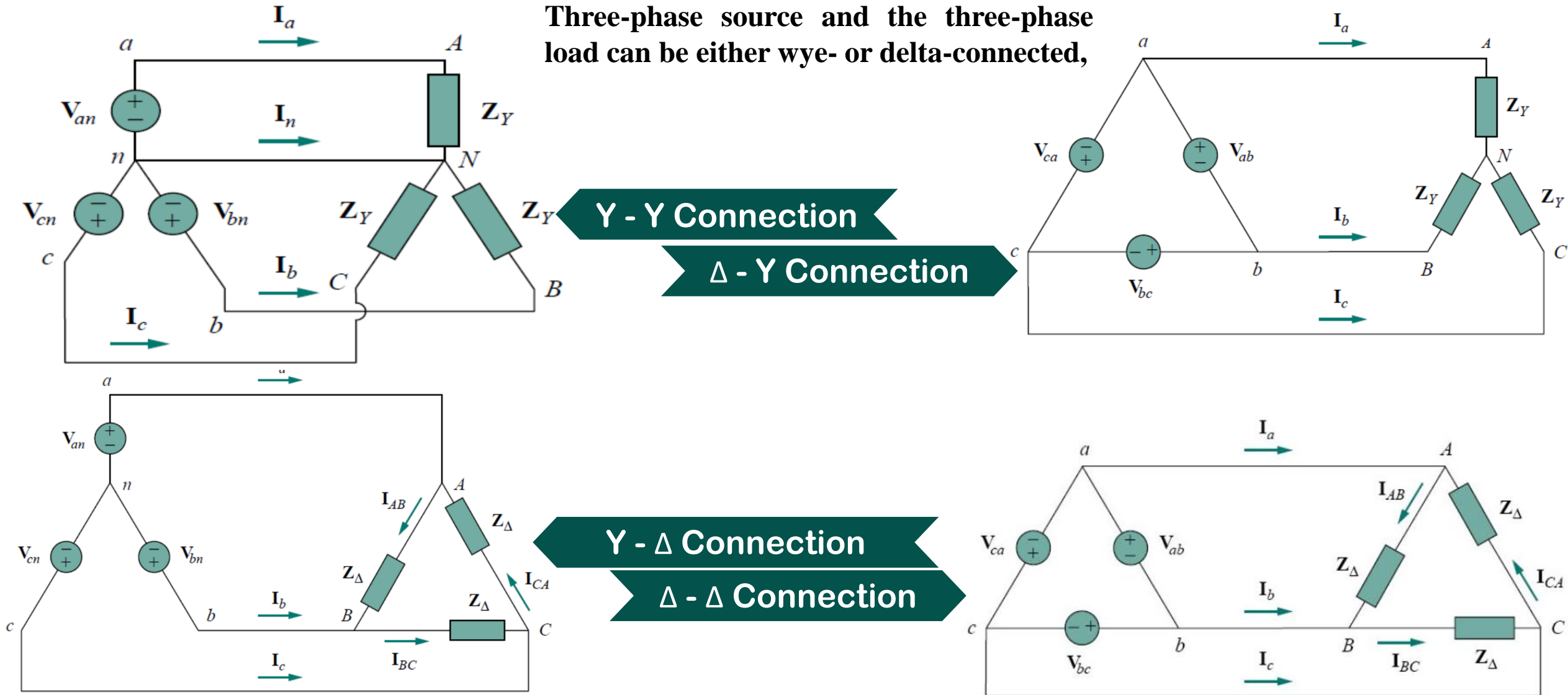
# Three phase systems

Three-phase source and the three-phase load can be either wye- or delta-connected,





# Three phase systems

## Three Phase Power

Total Power,  $P = 3 \times \text{Power in each phase}$

### Y-System

$$P = 3 \times V_{Ph} I_{Ph} \cos \phi$$

$$V_{Ph} = \frac{V_L}{\sqrt{3}} \quad I_{Ph} = I_L$$

$$P = 3 \times \frac{V_L}{\sqrt{3}} \times I_L \times \cos \phi$$

$$\text{Real Power } P = \sqrt{3} V_L I_L \cos \phi$$

$$\text{Reactive Power, } Q = \sqrt{3} V_L I_L \sin \phi$$

$$\text{Apparent Power, } S = \sqrt{3} V_L I_L = \sqrt{P^2 + Q^2}$$

$$\text{Power Factor} = \cos \phi = \frac{P}{S}$$

For balanced condition  $\mathbf{I}_N = \mathbf{I}_R + \mathbf{I}_Y + \mathbf{I}_B = 0$

### $\Delta$ -System

$$P = 3 \times V_{Ph} I_{Ph} \cos \phi$$

$$V_{Ph} = V_L \quad I_{Ph} = \frac{I_L}{\sqrt{3}}$$

$$P = 3 \times V_L \times \frac{I_L}{\sqrt{3}} \times \cos \phi$$

$$\text{Real Power } P = \sqrt{3} V_L I_L \cos \phi$$

$$\text{Reactive Power, } Q = \sqrt{3} V_L I_L \sin \phi$$

$$\text{Apparent Power, } S = \sqrt{3} V_L I_L = \sqrt{P^2 + Q^2}$$

$$\text{Power Factor} = \cos \phi = \frac{P}{S}$$



**Thank You !**