

BASIC ELECTRICAL ENGINEERING

Course Code: EE100



Dr. Pragnyashree Ray


Assistant Professor

Dept. of Electrical Engineering,

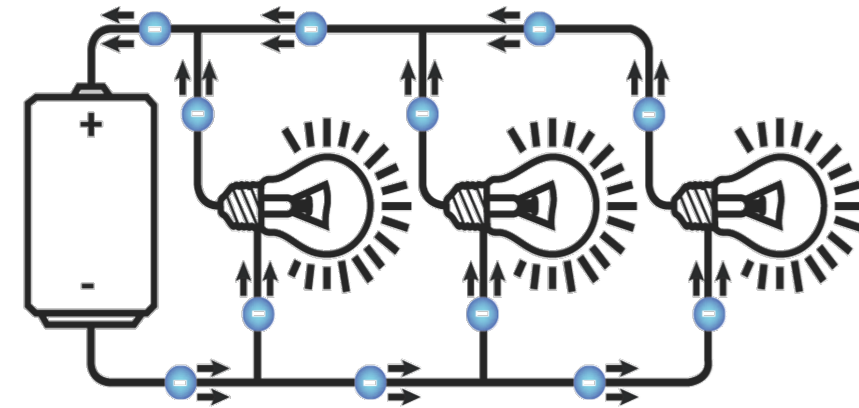C. V. Raman Global University, Bhubaneswar, Odisha

Module 1: DC Circuits


- ❖ Star-Delta Conversion
- ❖ KCL and KVL
- ❖ Series and Parallel Circuits
- ❖ Nodes, Branch, Loops and Mesh
- ❖ Voltage Source – Current Source Conversion




Star-Delta Conversion

T-connected and Equivalent Star Network

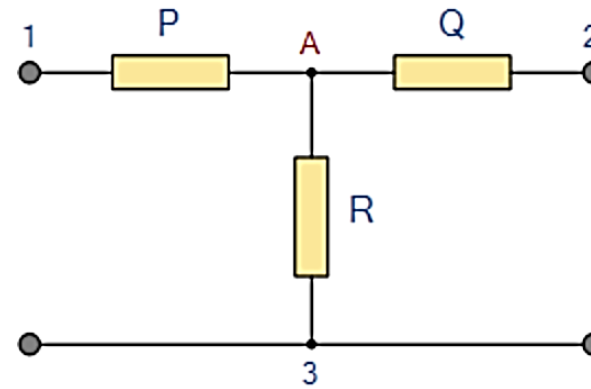We can redraw the T resistor network above to produce an electrically equivalent **Star** or Y type network




T-Network

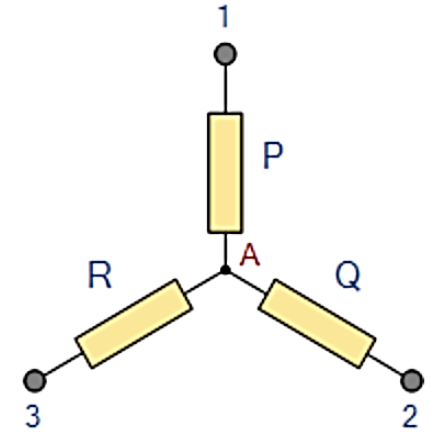

Star-Network


Δ -connected and Equivalent Delta Network

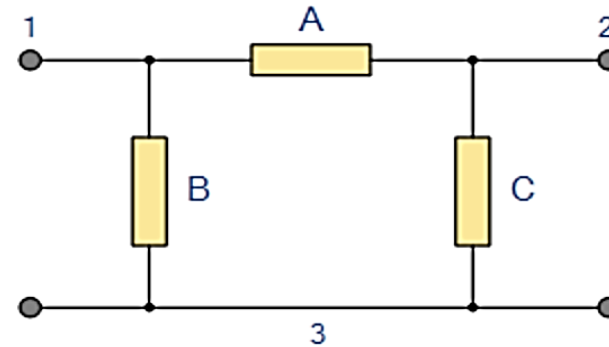We can also convert a Pi or π type resistor network into an electrically equivalent **Delta** or Δ type network as shown




Pi-Network

\equiv

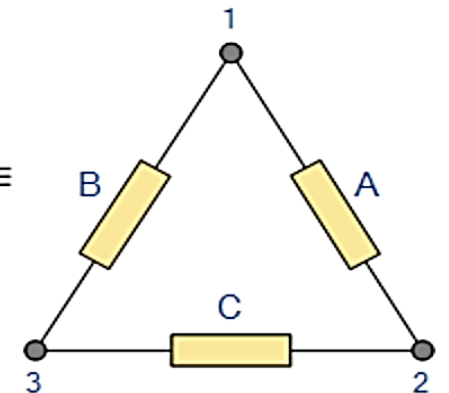

Delta-Network


Delta- Star Conversion & Vice-Versa

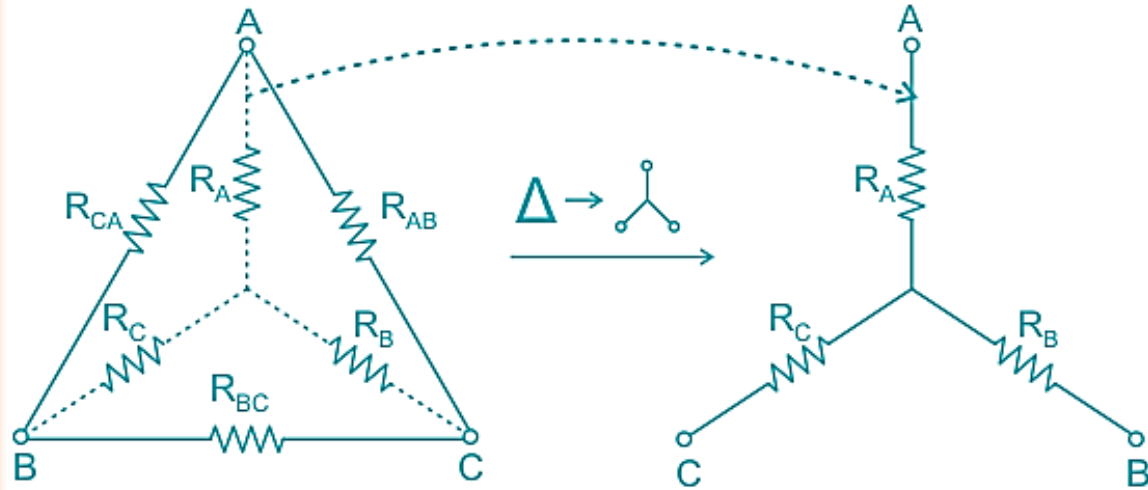

$$R_A = \frac{R_{AB} \cdot R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_B = \frac{R_{AB} \cdot R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$
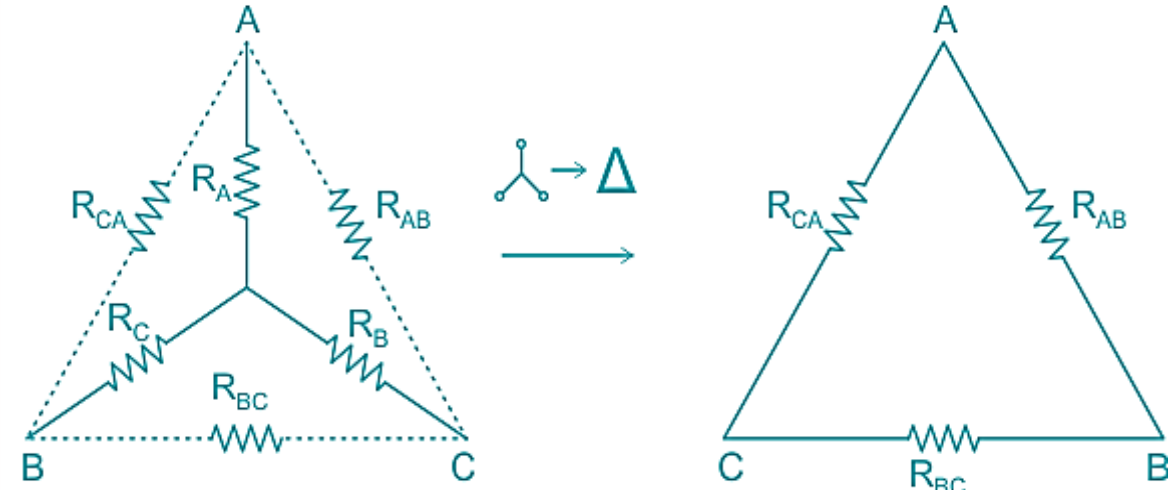
$$R_C = \frac{R_{BC} \cdot R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$




$$R_{AB} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$

$$R_{BC} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

$$R_{CA} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

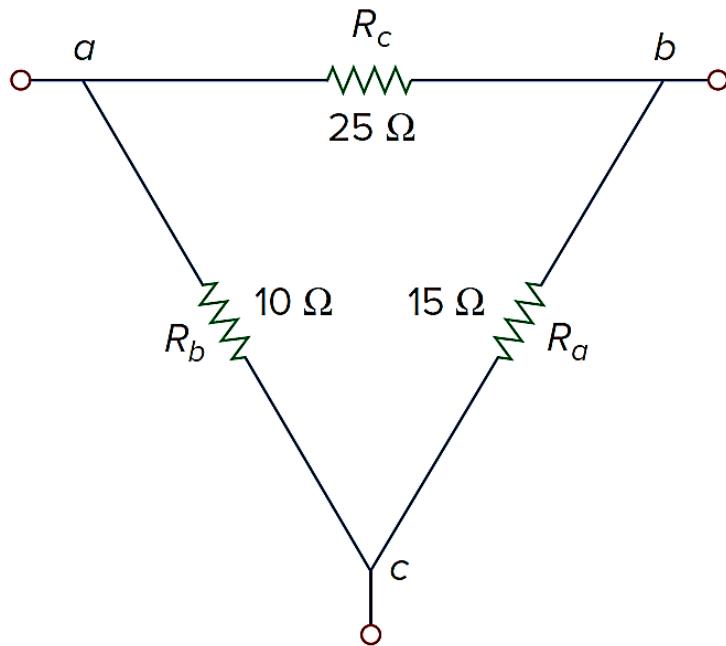Q1:

Convert the Δ network in Fig. below to an equivalent Y network




Solution:

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{10 \times 25}{15 + 10 + 25} = \frac{250}{50} = 5 \Omega$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} = \frac{25 \times 15}{50} = 7.5 \Omega$$
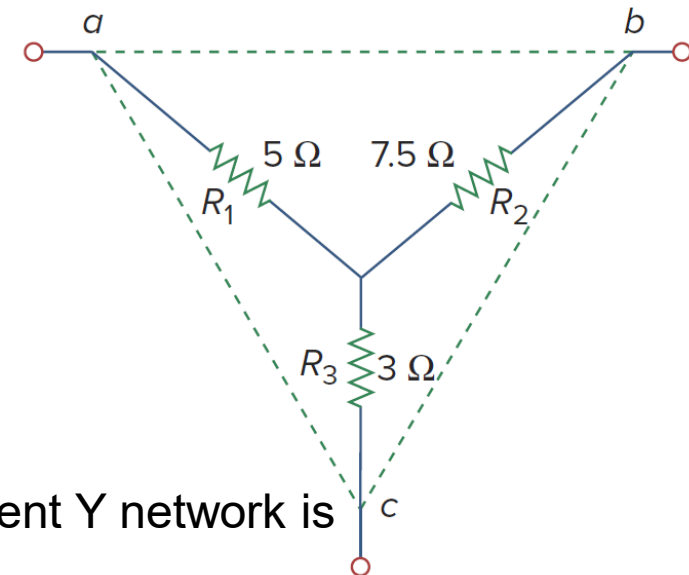
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{15 \times 10}{50} = 3 \Omega$$




The equivalent Y network is

Numericals:

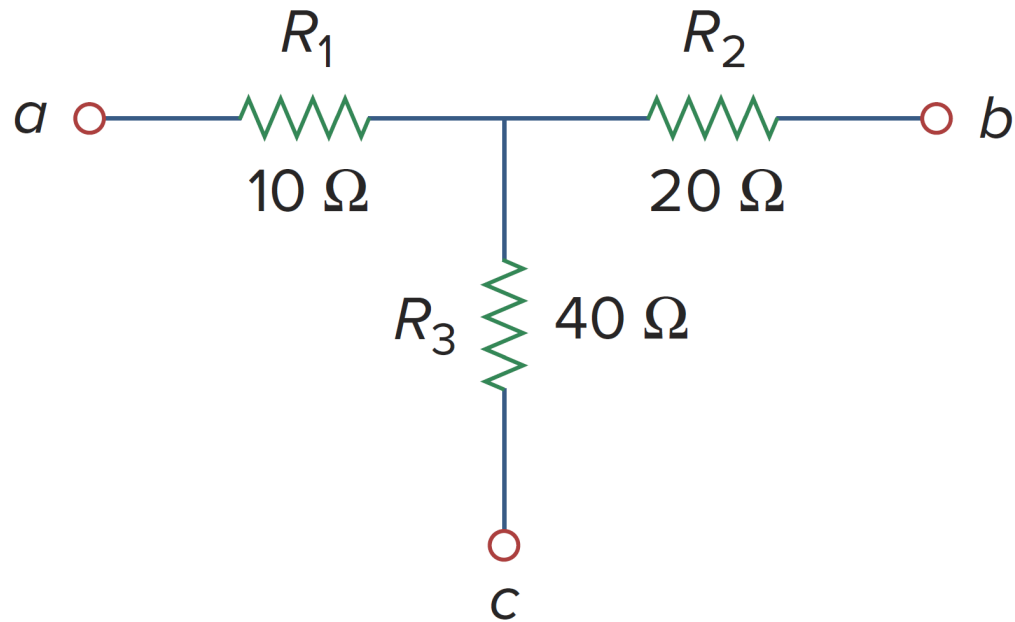Q2:


Convert the Y network in Fig. below to an equivalent Δ network



Answer: $R_a = 140\ \Omega$, $R_b = 70\ \Omega$, $R_c = 35\ \Omega$.

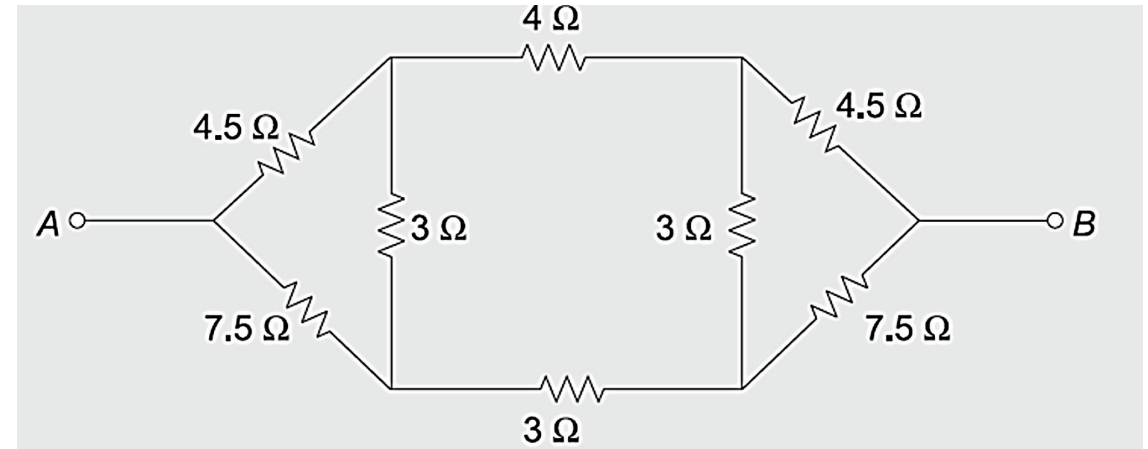Q3:






Find the equivalent resistance between A & B



Numericals: Home Work

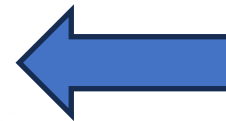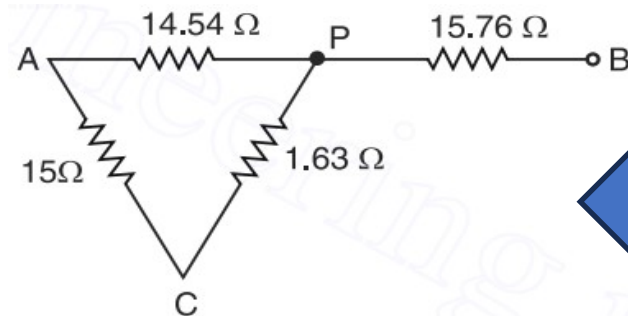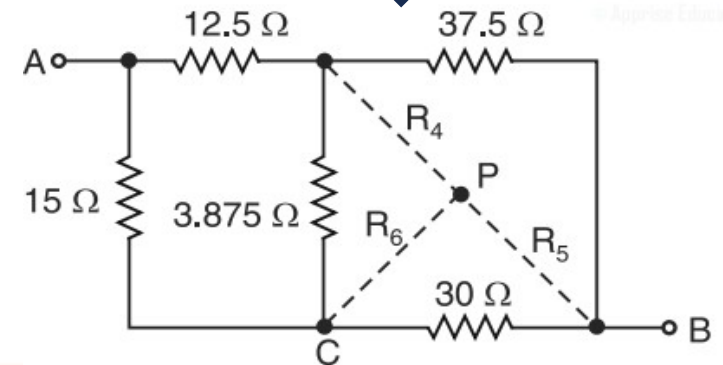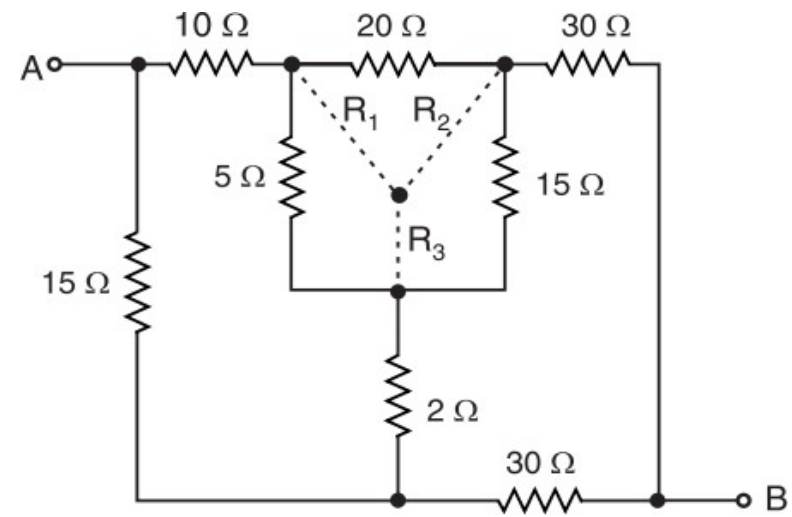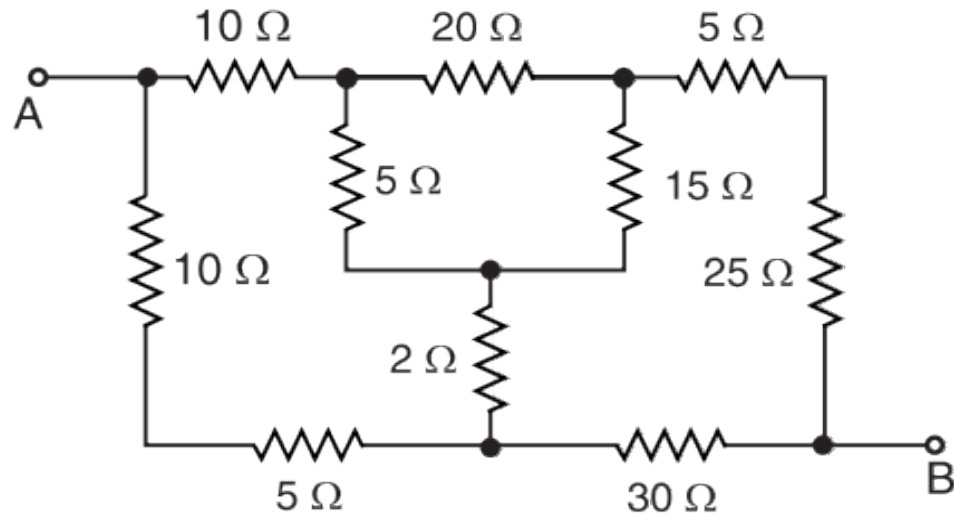Q4:

Find the equivalent resistance between A & B




$$R_{AB} = 15.76 + [14.54 \parallel (15 + 1.63)] = 15.76 + \frac{14.54 \times 16.63}{31.17} = 23.5\ \Omega$$

Node, Branch, Loop & Mesh:




Circuit Topology

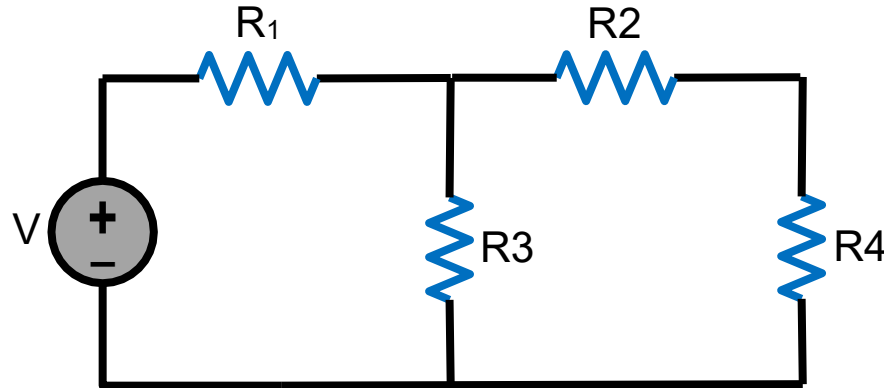


Node

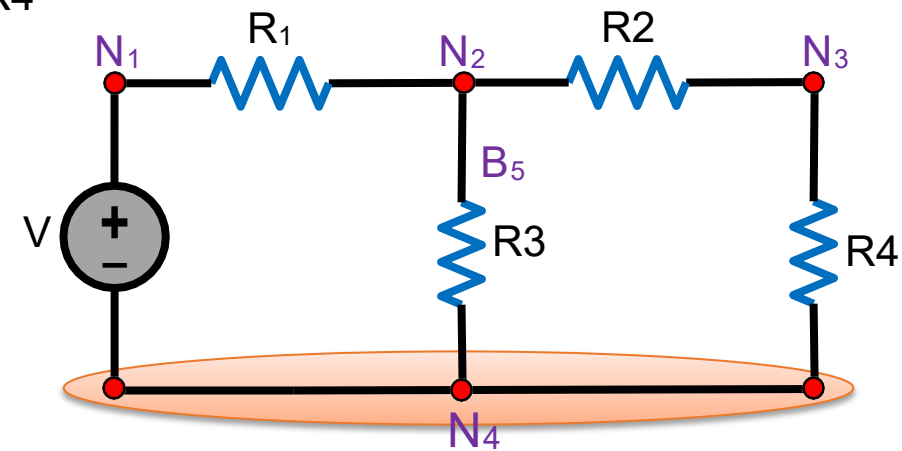A point or junction where two or more circuit's elements meet is called Node.



Branch

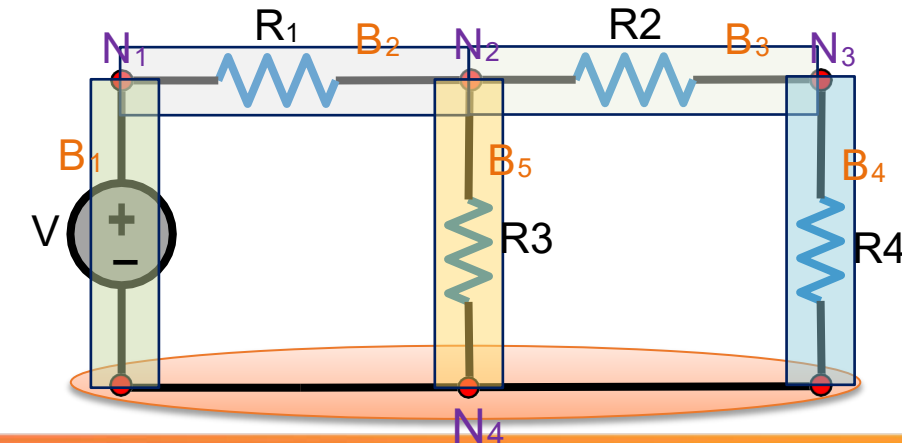That part or section of a circuit which locate between two junctions is called the branch.



Node, Branch, Loop & Mesh:


Circuit Topology

Loop

A closed path in a circuit is called as Loop.

Mesh

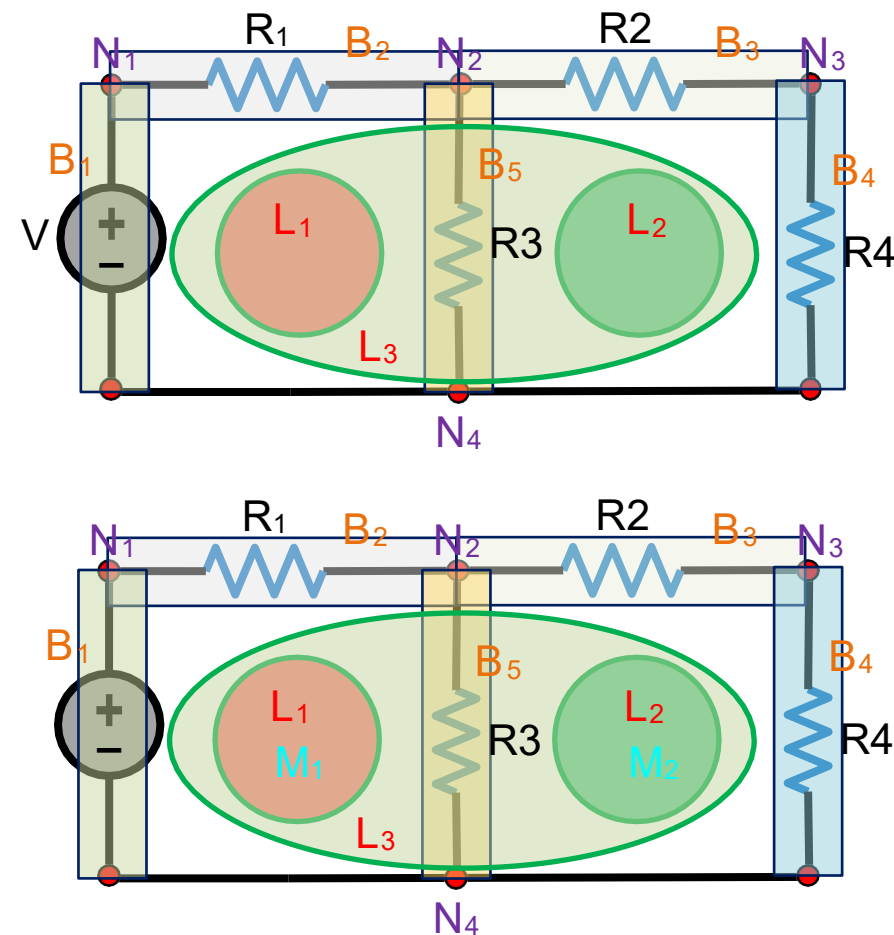
A closed loop which contains no other loop within it or a path which does not contain on other paths is called Mesh




Numericals:

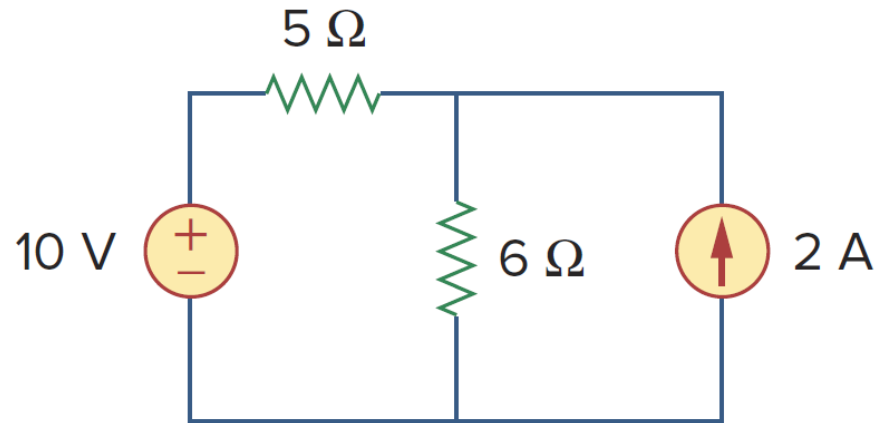Q1:

Determine the number of branches and nodes in the circuit shown in Fig. Identify which elements are in series and which are in parallel.



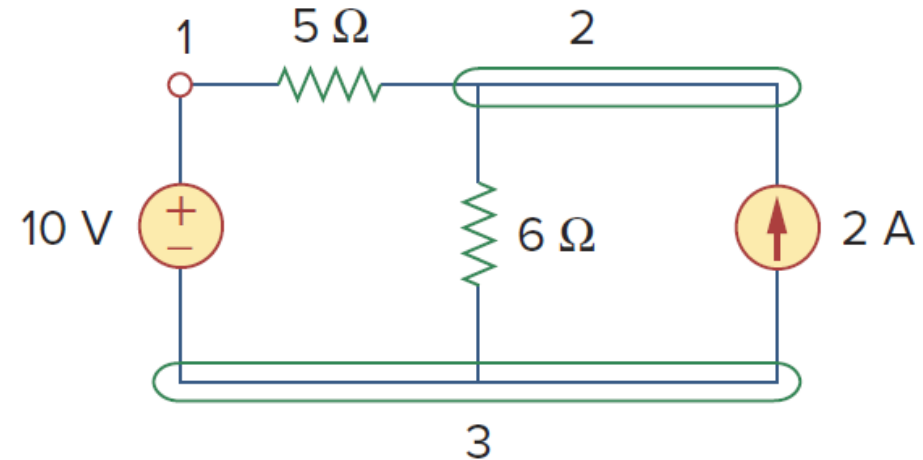Since there are four elements in the circuit, the circuit has four branches: 10 V, $5\ \Omega$, $6\ \Omega$, and 2 A.





Ans: 4 Branches, 3 Nodes

Numericals: Home Work

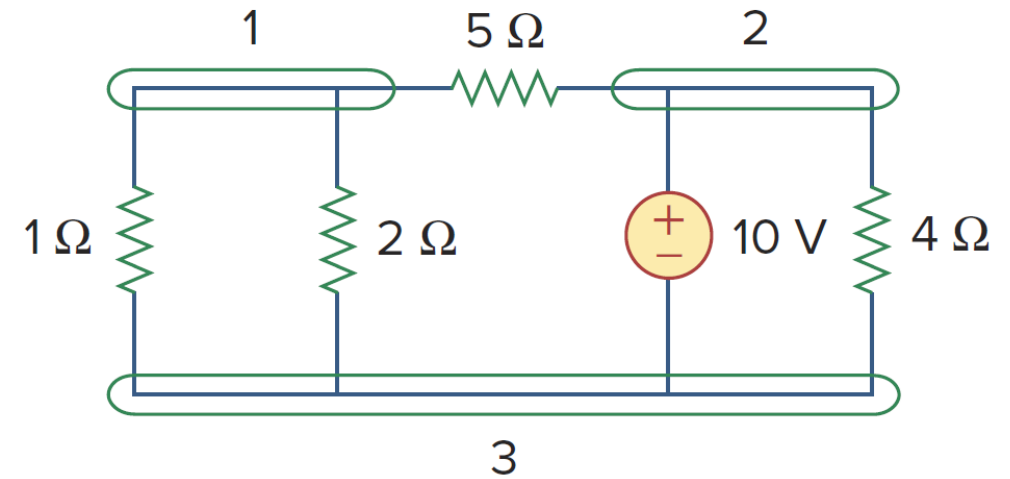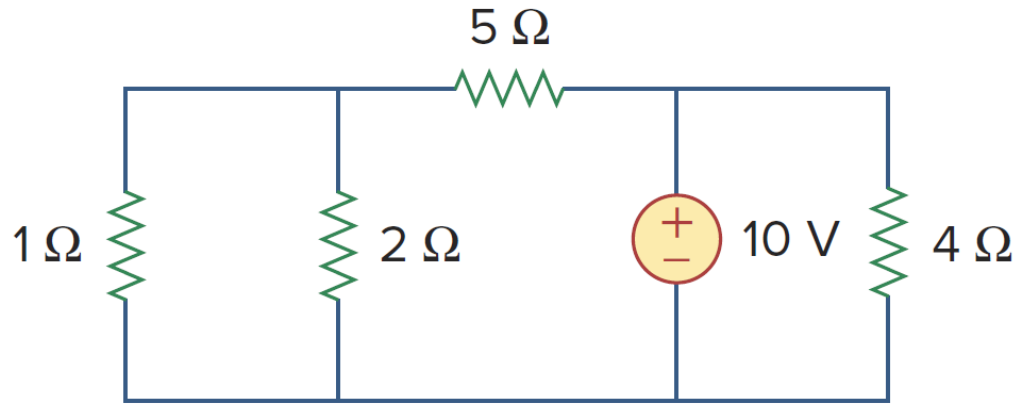Q2:

Determine the number of branches and nodes in the circuit shown in Fig. Identify which elements are in series and which are in parallel.



Series & Parallel Circuits


Circuit Topology

Series

Two or more elements are in series if they are cascaded or connected sequentially and consequently carry the same current.


Parallel

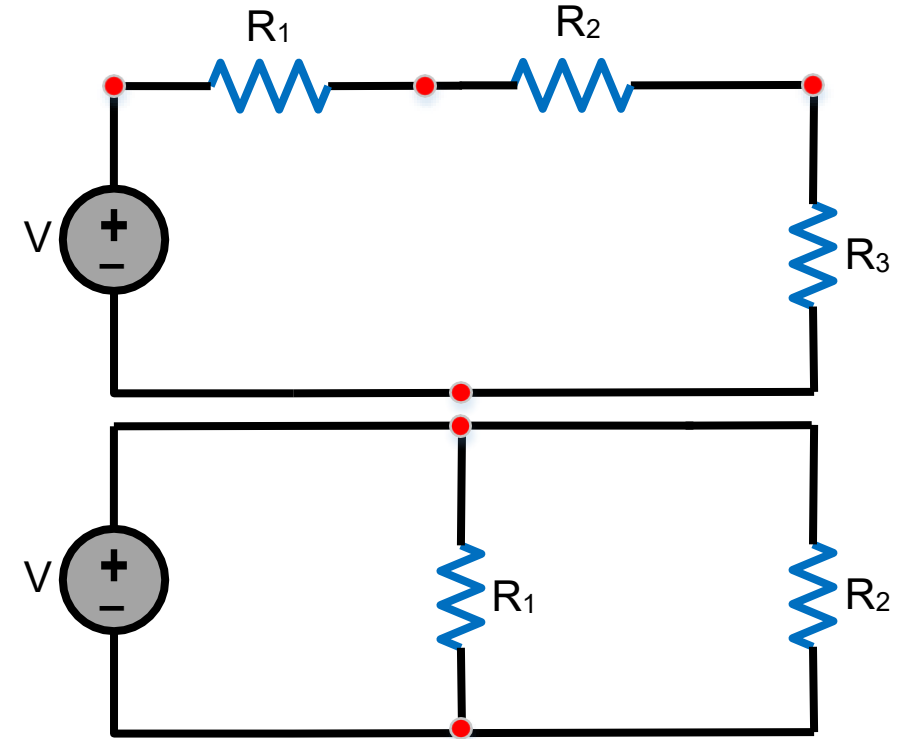Two or more elements are in parallel if they are connected to the same two nodes and consequently have the same voltage across them.




Kirchhoff's Law

Kirchhoff's Law

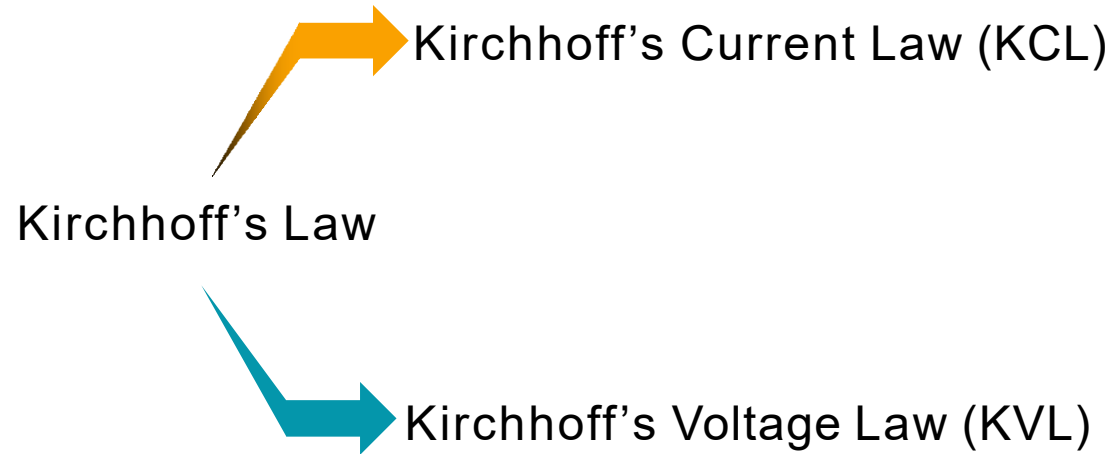

Kirchhoff's Current Law (KCL)

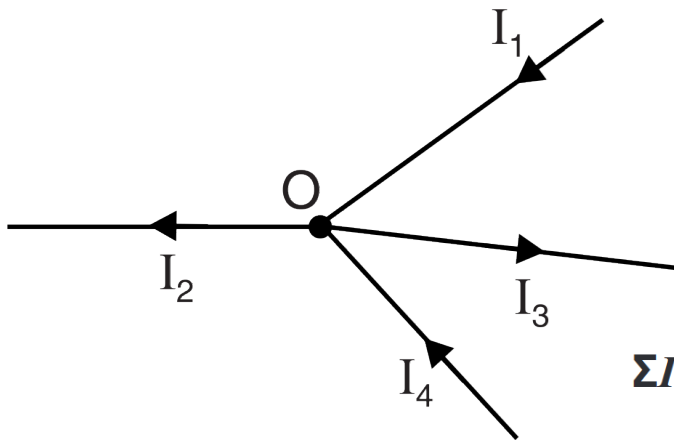The algebraic sum of the currents meeting at a junction in an electrical circuit is zero.



$$(I_1) + (I_4) + (-I_2) + (-I_3) = 0$$

$$I_1 + I_4 = I_2 + I_3$$

ΣI Entering = ΣI Leaving Sum of incoming currents = Sum of outgoing currents


Kirchhoff's Law

Kirchhoff's Law

Kirchhoff's Voltage Law (KVL)

In any closed electrical circuit or mesh, the algebraic sum of all the electromotive forces (e.m.fs) and voltage drops in resistors is equal to zero.

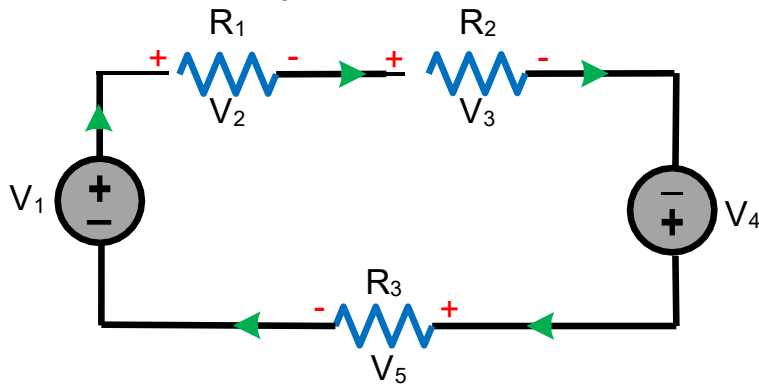
In any closed circuit or mesh, *Algebraic sum of e.m.fs + Algebraic sum of voltage drops = 0*




$$+V_1 - V_2 - V_3 + V_4 - V_5 = 0$$

$$V_2 + V_3 + V_5 = V_1 + V_4$$

$$V_{ab} = V_1 + V_2 - V_3$$

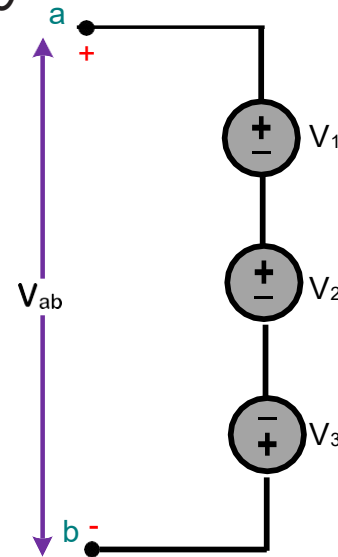


Series connection

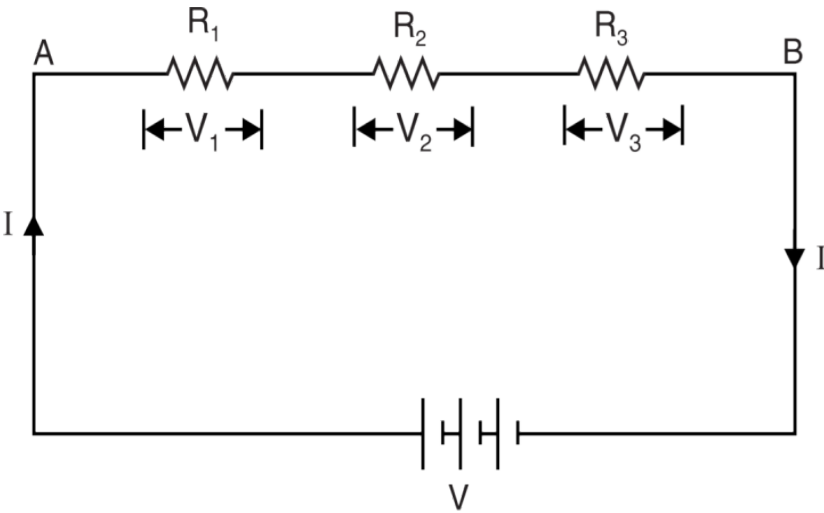


By Ohm's law, voltage across the various resistances is

$$V_1 = IR_1; V_2 = IR_2; V_3 = IR_3$$

$$V = V_1 + V_2 + V_3$$

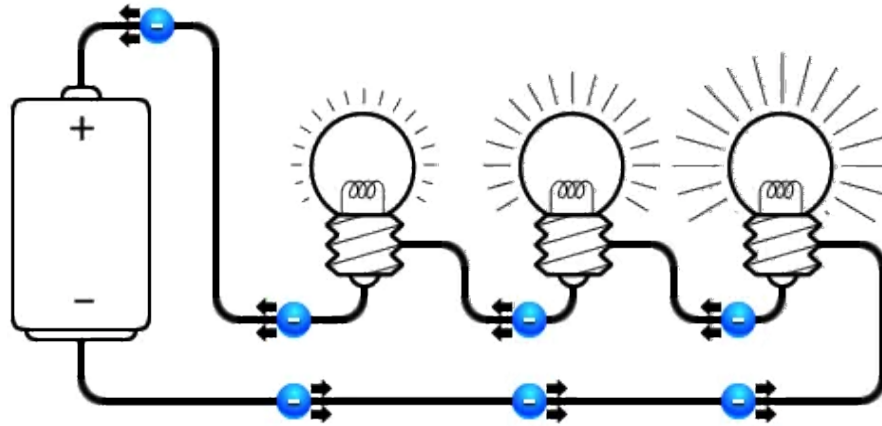


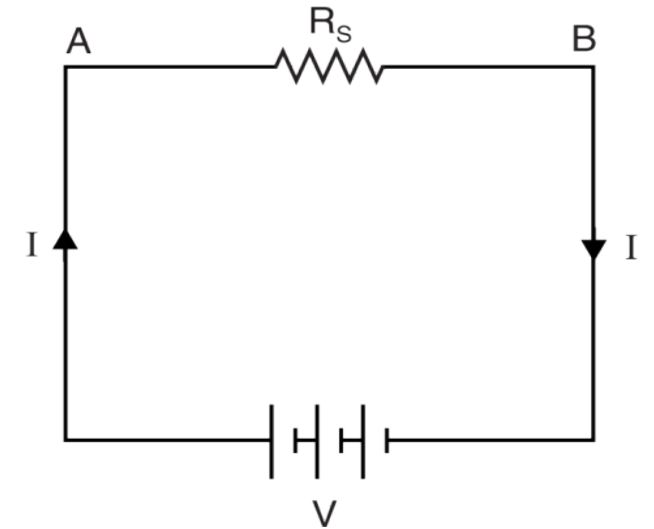
$$V = IR_1 + IR_2 + IR_3$$
$$V = I[R_1 + R_2 + R_3]$$



$$R_S = R_1 + R_2 + R_3$$

Hence when a number of resistances are connected in series, the total resistance is equal to the sum of the individual resistances

Parallel connection

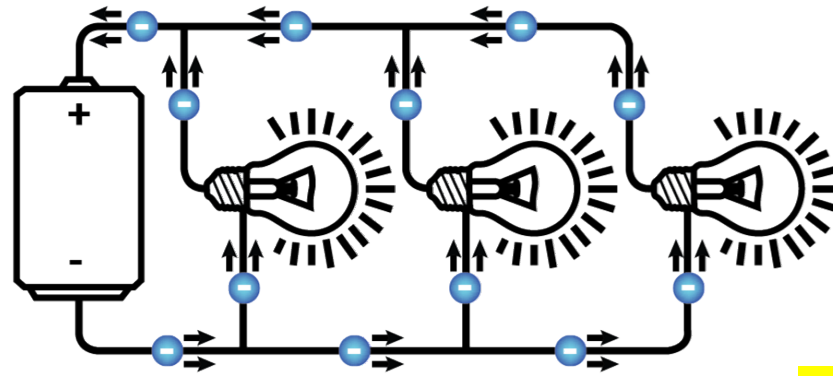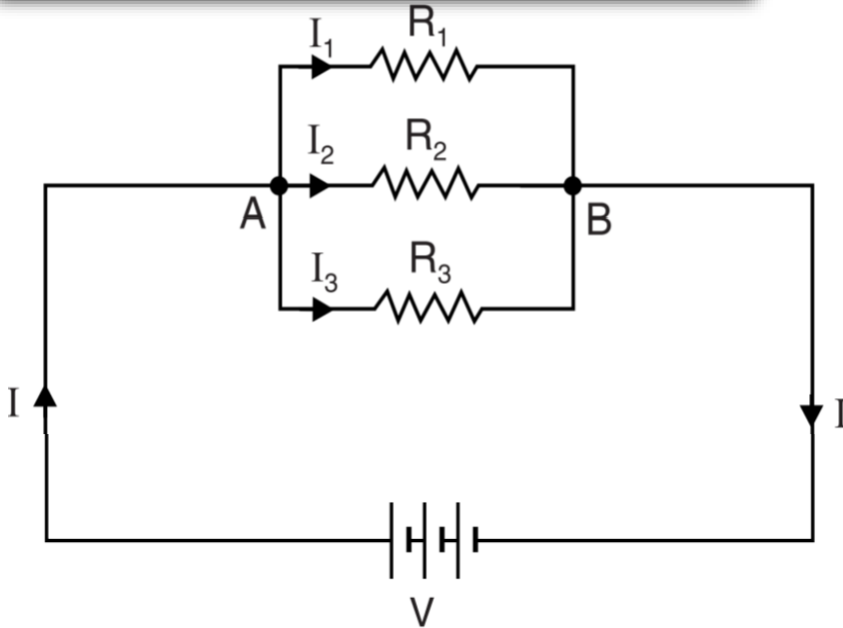

Two Resistances in Parallel

$$I = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$\frac{I}{V} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_P} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Hence when a number of resistances are connected in parallel, the reciprocal of total resistance is equal to the sum of the reciprocals of the individual resistances

Series circuit

Parallel network

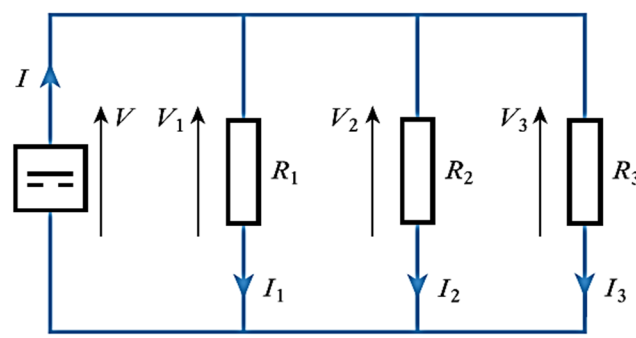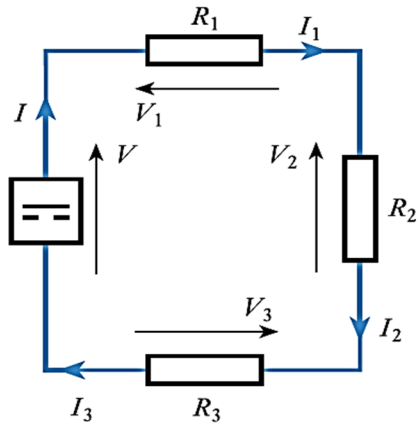

Current

The current is the same in all parts of the circuit

$$I = I_1 = I_2 = I_3$$

The total current supplied to the network equals the sum of the currents in the various branches

$$I = I_1 + I_2 + I_3$$

Voltage

The total voltage equals the sum of the voltages across the different parts of the circuit

$$V = V_1 + V_2 + V_3$$

The voltage across a parallel combination is the same as the voltage across each branch

$$V = V_1 = V_2 = V_3$$

Resistance


The total resistance equals the sum of the separate resistances

$$R = R_1 + R_2 + R_3$$

The reciprocal of the equivalent resistance equals the sum of the reciprocals of the branch resistances

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Voltage Division Rule

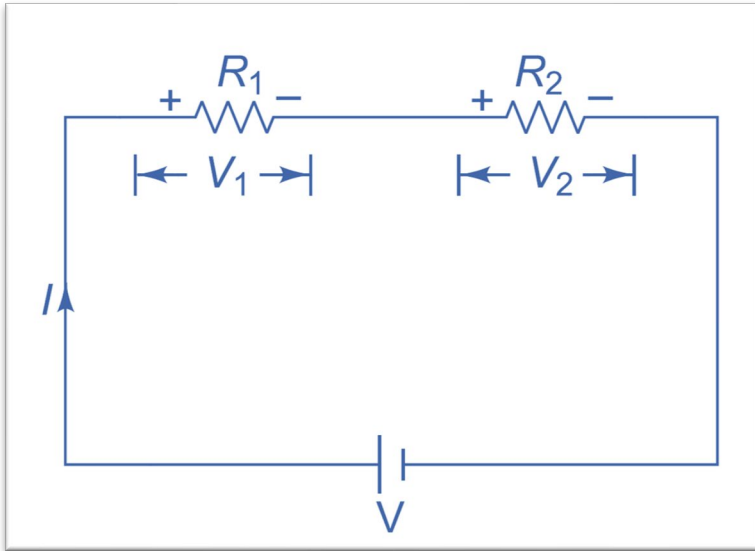


Voltage Division in a Series Circuit

$$I = \frac{V}{R_1 + R_2}$$

Hence, voltage across $R_1 = V_1 = R_1 I = R_1 \frac{V}{R_1 + R_2} = \frac{R_1}{R_1 + R_2} V$

Similarly, voltage across $R_2 = V_2 = R_2 I = R_2 \frac{V}{R_1 + R_2} = \frac{R_2}{R_1 + R_2} V$

Current Division Rule

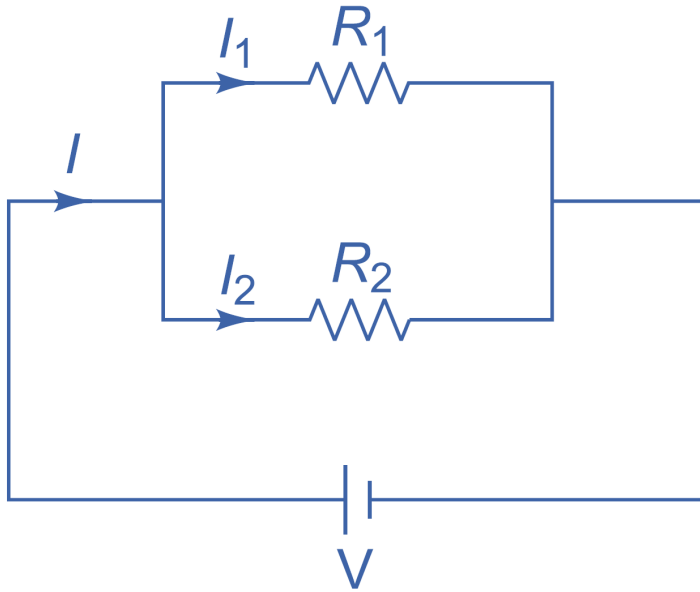

Current Division in a Parallel Circuit

Case (i) When two resistances are connected in parallel,

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

Also,

$$V = R_T I = R_1 I_1 = R_2 I_2$$

$$\text{Hence, current through } R_1 = I_1 = \frac{V}{R_1} = \frac{R_T I}{R_1} = \frac{R_2}{R_1 + R_2} I$$

$$\text{Similarly, current flowing through } R_2 = I_2 = \frac{V}{R_2} = \frac{R_T I}{R_2} = \frac{R_1}{R_1 + R_2} I$$

Source Transformation

- ❖ A voltage source with a series resistor can be converted into an equivalent current source with a parallel resistor.
- ❖ Conversely, a current source with a parallel resistor can be converted into a voltage source with a series resistor.

